

Logic Lab – Exp #6

Combinational Circuit Synthesis

Y-0016/001D and Y-0016/005D board (given in next page)

1) The half adder adds two single binary digits A and B. It has two outputs, sum (**S**) and carry (**C**). The carry signal represents an overflow into the next digit of a multi-digit addition. Fill in the truth table for a half adder and design the circuit. Then use modular half adder circuit (with EXOR gate) and verify results with your circuit.

2) A full adder adds binary numbers and accounts for values carried in as well as out. A one-bit full-adder adds three one-bit numbers, often written as **A**, **B**, and **C_{in}**; **A** and **B** are the operands, and **C_{in}** is a bit carried in from the previous less-significant stage.

The circuit produces a two-bit output, carry and sum typically represented by the signals **C_{out}** and **S**.

First formulate the truth table with **A**, **B**, **C_{in}** as inputs, and **C_{out}**, **S** as outputs.

Then design the circuit with logic gates. Then use modular full adder circuit (with EXOR gate) and verify your results.

3) The half subtractor is a circuit which is used to perform subtraction of two bits. It has two inputs, **X** and **Y**; and two outputs the difference **D = X - Y** and borrow out **B_{out}**.


The borrow out signal is set when the subtractor needs to borrow from the next digit in a multi-digit subtraction. That is, when $X < Y$. Since X and Y are bits, if and only if $X = 0$ and $Y = 1$.

Fill in the truth table for a half subtractor and design the circuit.


Then implement the circuit using modular full adder circuit.

Logic Lab – Exp #6



Modular Half Adder Circuit

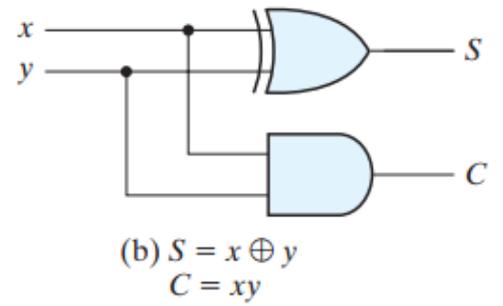

Modular Full Adder Circuit

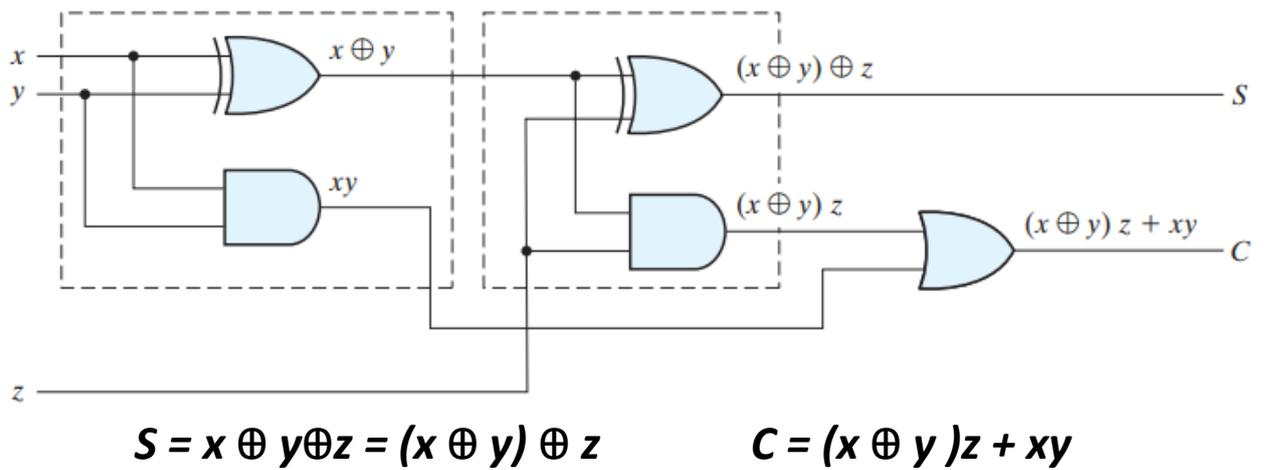

Subtractor Using Full Adder Circuit

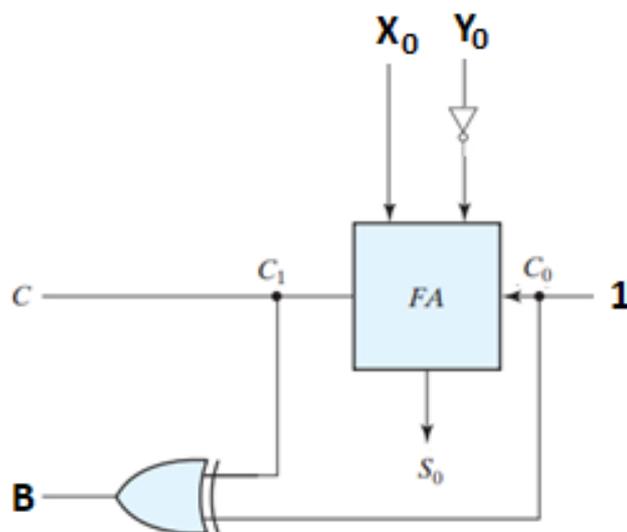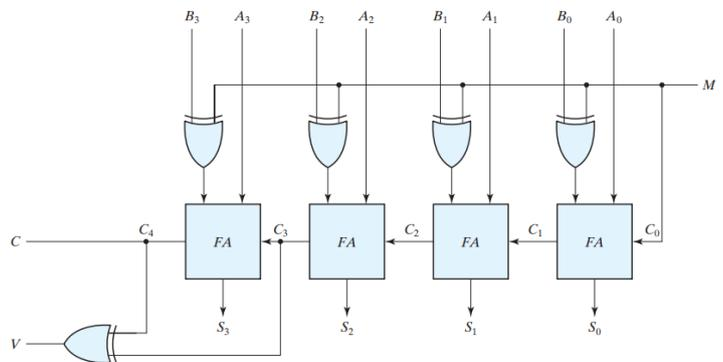

Logic Lab – Exp #6

