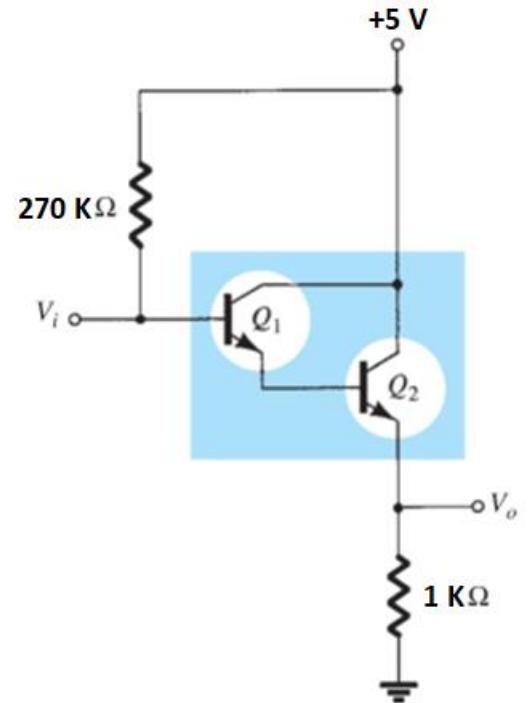


# EXPERIMENT 5

## DC Analysis of Multistage BJT configurations

Setup the given **Darlington pair** circuit using the **BC237** transistors.

- 1.1.** Measure the base current  $I_{B1}$ , collector current  $I_{C2}$  and collector-emitter voltage  $V_{CE2}$ .




- 1.2.** Calculate same parameters using DC analysis theoretically.

# EXPERIMENT 5

## DC Analysis of Multistage BJT configurations

Setup the given **Cascode** circuit using the **BC237** transistors.

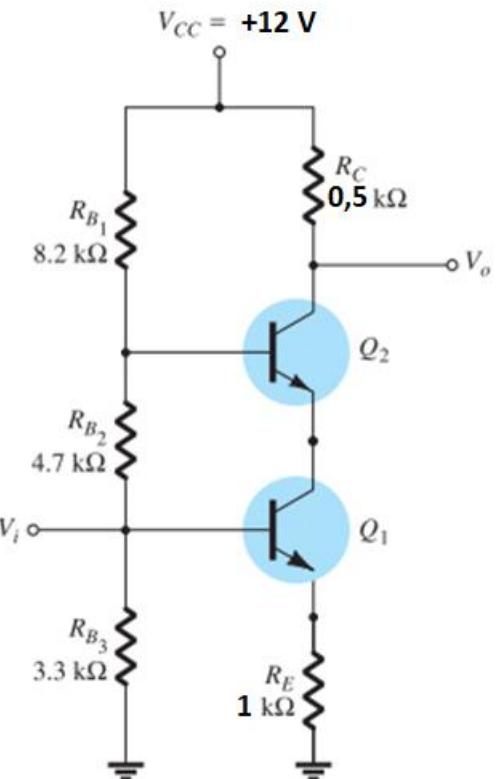- 2.1. Measure the collector current  $I_C$  and voltages  $V_{B1}$ ,  $V_{B2}$ ,  $V_{E1}$ ,  $V_{C1}$ ,  $V_{C2}$ , and  $V_o$ .



- 2.2. Calculate same parameters using DC analysis theoretically.




# EXPERIMENT 5

## DC Analysis of Multistage BJT configurations

Setup the given **Cascade** circuit using the **BC237** transistors.

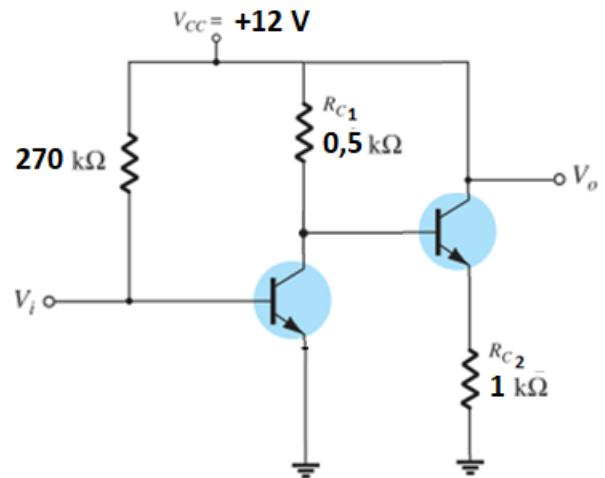- 3.1. Measure the emitter current  $I_E$ , collector current  $I_C$ , base voltage  $V_B$ , collector-emitter voltage  $V_{CE}$ .



- 3.2. Calculate same parameters using DC analysis theoretically.

