

# **ELECTRONICS LABORATORY**

## **PART 8 EXPERIMENTS**

**Assoc. Prof. Serhan Yarkan**

**ISTANBUL COMMERCE UNIVERSITY**


## Contents

<b>EXPERIMENT 8.1</b> .....	<b>2</b>
DERIVING INPUT CHARACTERISTICS OF E-VMOSFET .....	2
<b>EXPERIMENT 8.2</b> .....	<b>4</b>
DERIVING OUTPUT CHARACTERISTICS OF E-VMOSFET .....	4
<b>EXPERIMENT 8.3</b> .....	<b>6</b>
EXAMINATION OF E-VMOSFET'S OPERATION .....	6

# EXPERIMENT 8.1

## DERIVING INPUT CHARACTERISTICS OF E-VMOSFET


**EXPERIMENTAL PROCEDURE:** Plug the Y-0016/013 smodule. Make the circuit connections as in figure 8.1.

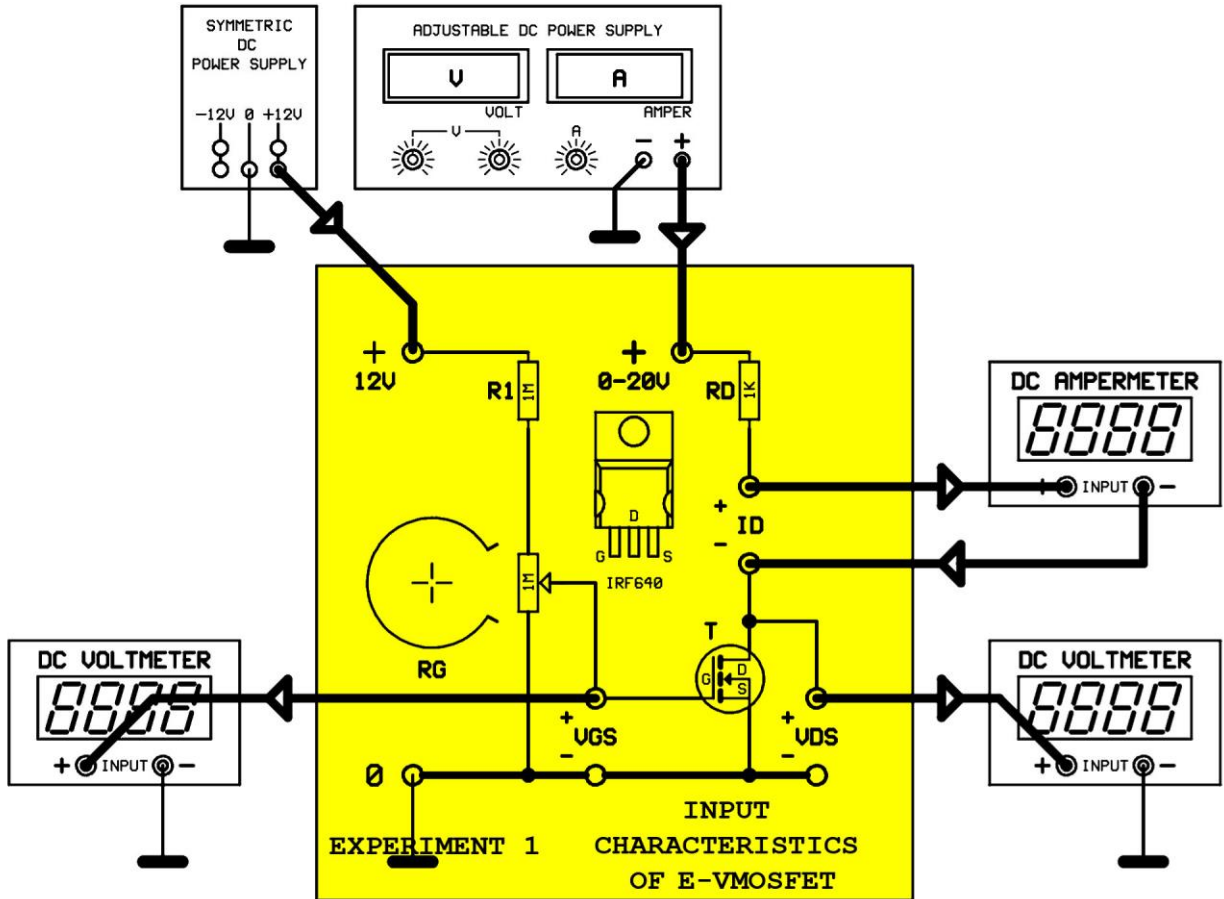

**Figure 8.1**

- 1-** Adjust the VGS voltage to zero with the help of RG potentiometer. Then, adjust **VDD=VDS** voltage to 20Volt in power supply.
- 2-** Adjust the VGS voltage to the values in table in figure 8.2 by the help of RG potentiometer. Type the drain current (**ID**) at each step. Draw the VGS-ID curve.

VDD=20V CONSTANT			
VGS (VOLT)	ID (mA)	VGS (VOLT)	ID (mA)
0.0		3.1	
2.0		3.2	
2.5		3.3	
2.8		3.4	
2.9		3.5	
3.0		4.0	

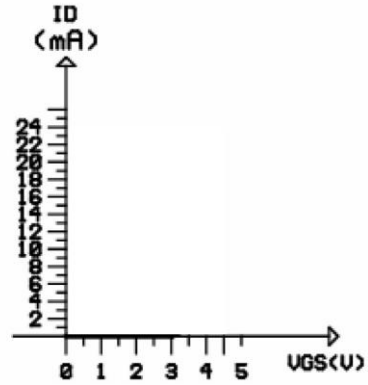

**Figure 8.2**

**3-** At which VGS values did the E-VMOSFET start transmission and reach saturation?

To transmission at **VGS**=.....Volt, to saturation at **VGS**=.....Volt

**4-** How much is the drain current (**ID**) at saturation? Why?

**ID**=.....mA. The reason is .....

**5-** How much is the VDS voltage of E-VMOSFET at saturation? What happens to the resistance of E-VMOSFET at that moment?

It is **VDS**=.....mV at saturation. The reason is .....

**6-** Repeat the experiment after adjusting **VDD**=10Volt. Type drain currents (**ID**) of each step to table in figure 8.3.

VDD=10V CONSTANT			
VGS (VOLT)	ID (mA)	VGS (VOLT)	ID (mA)
0.0		3.1	
2.0		3.2	
2.5		3.3	
2.8		3.4	
2.9		3.5	
3.0		4.0	

**Figure 8.3**

**7-** What happened to transmission and saturation points of E-VMOSFET after changing the VDD voltage? Compare the new value with VGS value at **VDD**=20Volt.

To transmission at **VGS**=.....Volt and to saturation at **VGS**=.....Volt.  
Transmission and saturation points of VMOSFET .....

# EXPERIMENT 8.2

## DERIVING OUTPUT CHARACTERISTICS OF E-VMOSFET

**EXPERIMENTAL PROCEDURE:** Plug the Y-0016/013 module. Before making the circuit connections, adjust output voltage of power supply to "0" (rotate voltage potentiometer to left) and adjust gate voltage to "0" (rotate "RG" potentiometer to left). Make the circuit connections as in figure 8.4 and apply energy to circuit.

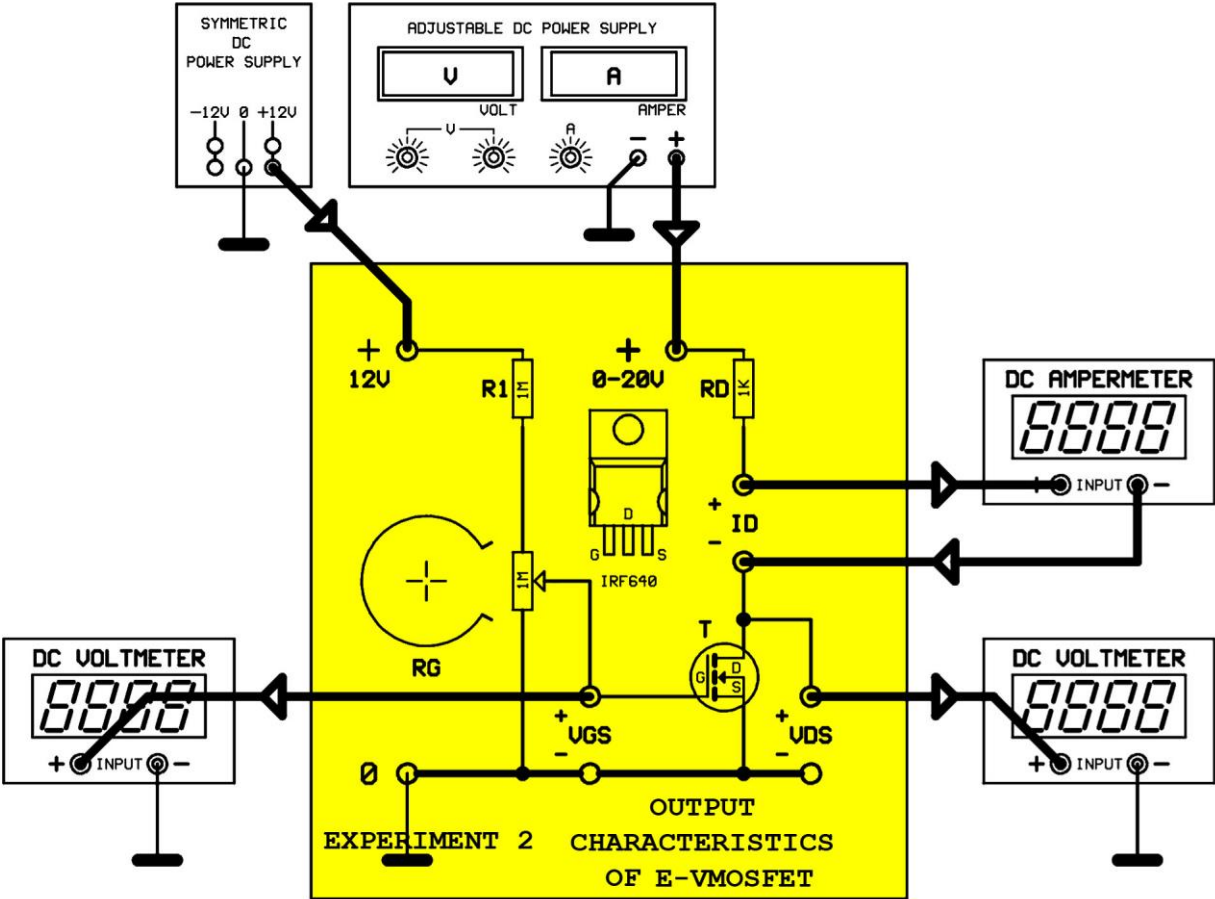


Figure 8.4

1- Adjust **VGS=0** by the help of "RG" potentiometers. Adjust the voltage of power supply to the values at the table in figure 8.5, respectively. Type the ID value at each step to the related section. Complete the table by adjusting to **VGS=2Volt**, **VGS=4Volt**, **VGS=5Volt**.

VGS=0 CONSTANT		VGS=2 CONSTANT		VGS=4 CONSTANT		VGS=5 CONSTANT	
VDD (VOLT)	ID (mA)	VDD (VOLT)	ID (mA)	VDD (VOLT)	ID (mA)	VDD (VOLT)	ID (mA)
1		1		1		1	
2		2		2		2	
3		3		3		3	
4		4		4		4	
5		5		5		5	
10		10		10		10	
15		15		15		15	
20		20		20		20	

Figure 8.5

2- Draw the change graphics between VDD-ID axes like in figure 8.6.

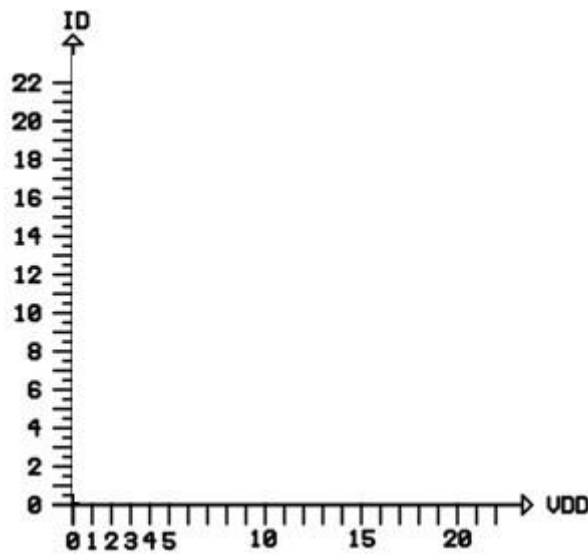


Figure 8.6


3- How is the change of VDD-ID?

4- What restricts the drain current?

# EXPERIMENT 8.3

## EXAMINATION OF E-VMOSFET'S OPERATION

**EXPERIMENTAL PROCEDURE:** Plug the Y-0016/013 module. Make the circuit connections as in figure 8.7.

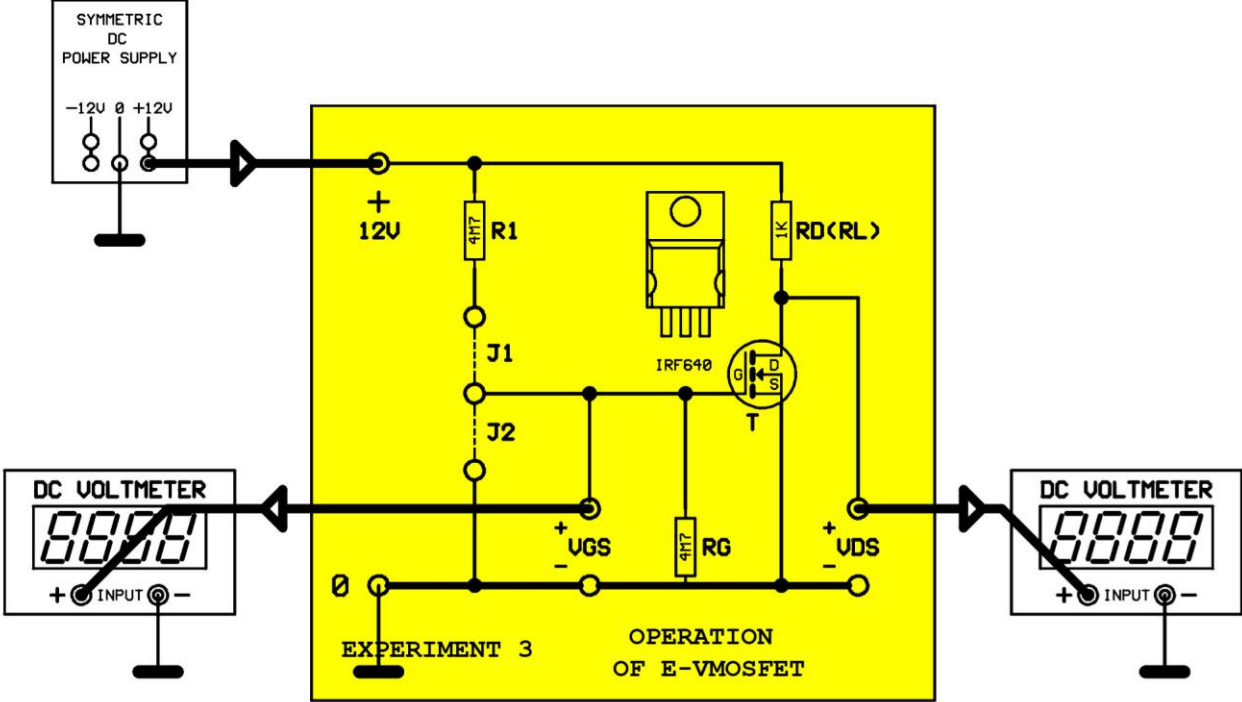

**Figure 8.7**

**1-** Short-circuit J2 points. Apply energy to the circuit. How much is the VDS voltage? Why?

**VDS**=.....Volt because .....

.....

**2-** Open the short-circuit on J2 points. Short-circuit J1 points. Measure the VGS and VDS voltages. In what situation (**cut off-transmission-saturation**) is E-VMOSFET at that moment?

**VGS**=.....Volt, **VDS**=.....mVolt. E-VMOSFET is at .....

**3-** What is the meaning of **VDS**=2mV at saturation point?

**VDS**=2mV at saturation point means that .....

.....