



ISTANBUL COMMERCE UNIVERSITY

DEPARTMENT OF ELECTRICAL-ELECTRONICS ENGINEERING

EEE202 ELECTRO-TECHNICH LABORATORY

**PART 7
EXPERIMENTS**

Contents

EXPERIMENT 7.1	3
EXAMINATION OF RL PARALLEL AC CIRCUIT	3
EXPERIMENT 7.2	6
EXAMINATION OF RC PARALLEL AC CIRCUIT	6

EXPERIMENT 7.1

EXAMINATION OF RL PARALLEL AC CIRCUIT

REQUIRED MATERIAL:

- 1- Function Generator
- 2- Oscilloscope (**two channeled**)
- 3- three AC ampermeters
- 4- Y-0016/01AC module
- 5- Enough connection cable

THE EXPERIMENT:

Adjust the terminal of the function generator to sine, peak to peak value to **E_{pp}=10V**olt and frequency to **F=1K**Hz. Connect the Y-0016/01AC module to its place. Make the circuit connections as in the figure 7.1. Apply the power to the circuit.

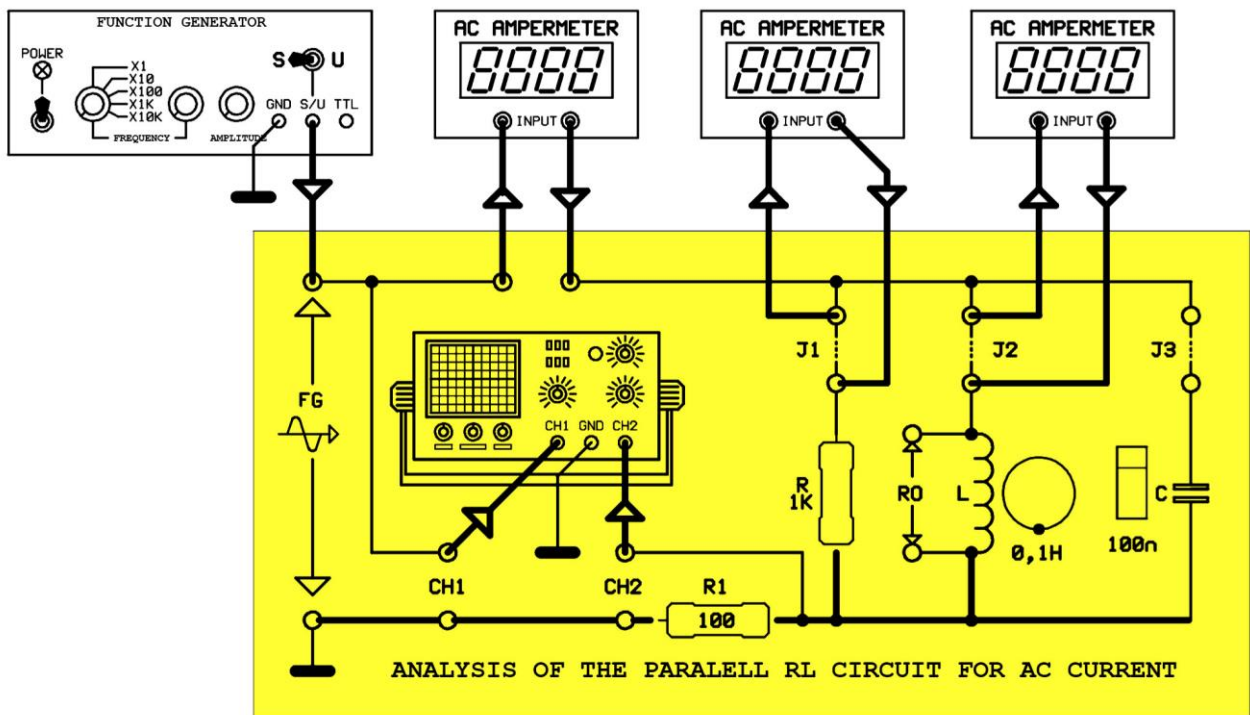


Figure 7.1

1- What can be said about the circuit looking at the vector diagram on the oscilloscope?

2- Short-circuit the CH2 points so that "R1" resistor will not affect the circuit.

3- Calculate the inductive reactance of the inductor

$$XL = 2\pi FL$$

4- Calculate the circuit current and currents passing through the legs of circuit.

$$IR = \frac{E}{R} =$$

$$IL = \frac{E}{XL} =$$

$$I = \sqrt{IR^2 + IL^2}$$

$$I =$$

5- Read the current values shown by Ampermeters. Compare the current values in Ampermeters with the calculated current values.

6- Draw the phasor diagram and the impedance triangle of the circuit.



Figure 7.2

7- Find the circuit impedance using the values in measurement devices.

$$Z = \frac{E}{I} =$$

8- Find the power coefficient and phase angle of the circuit.

$$\cos\varphi = \frac{IR}{I} =$$

$$\varphi =$$

9- Calculate the active power dissipated using the values in measurement devices.

$$P = E.I.\cos\varphi$$

$$P =$$

EXPERIMENT 7.2

EXAMINATION OF RC PARALLEL AC CIRCUIT

REQUIRED MATERIAL:

- 1- Function Generator
- 2- Oscilloscope (**two channeled**)
- 3- three AC ampermeters
- 4- Y-0016/01AC module
- 5- Enough connection cable

THE EXPERIMENT:

Adjust the terminal of the function generator to sine, peak to peak value to **E_{pp}**=10Volt and frequency to **F**=1KHz. Connect the Y-0016/01AC module to its place. Make the circuit connections as in the figure 7.3. Apply the power to the circuit.

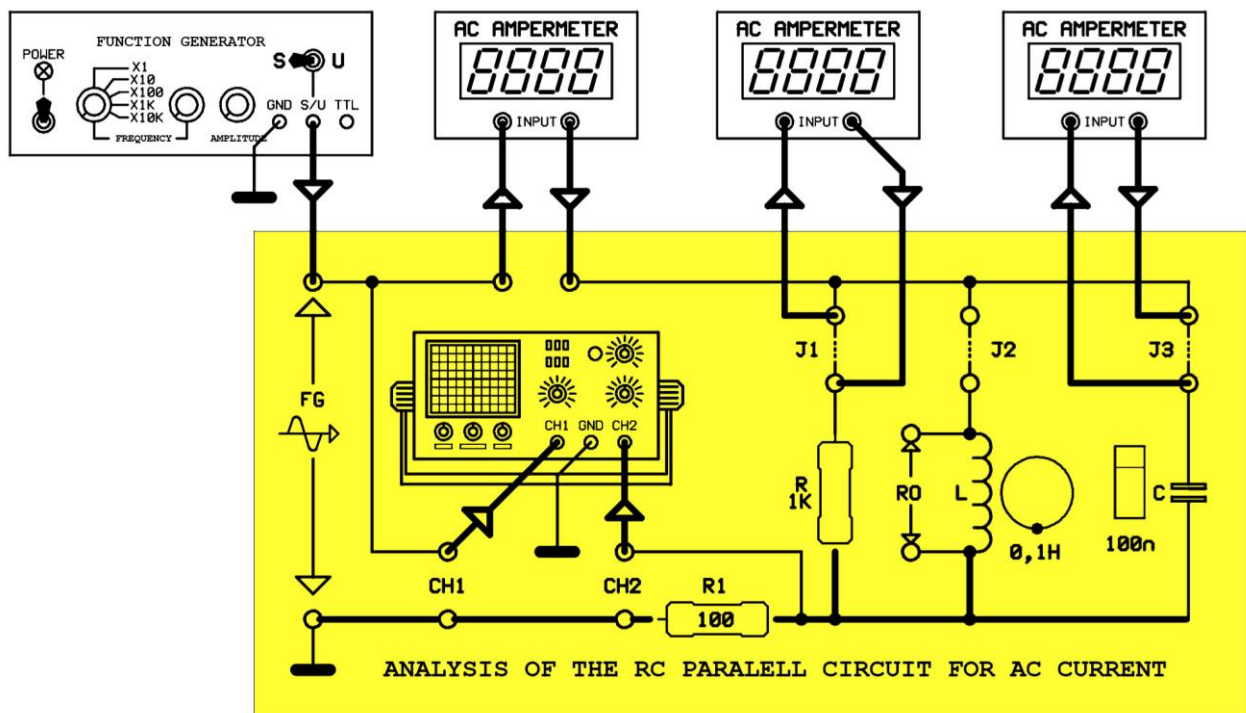


Figure 7.3

- 1- What can be said about the circuit looking at the vector diagram on the oscilloscope?

2- Short-circuit the CH2 points so that "**R1**" resistor will not affect the circuit.

3- Calculate the capacitive reactance of the capacitor.

$$XC = \frac{I}{2\pi FC}$$

$$XC =$$

4- Calculate the circuit current and currents passing through the legs of circuit

$$IR = \frac{E}{R} =$$

$$IL = \frac{E}{XC} =$$

$$I = \sqrt{IR^2 + IC^2}$$

$$I =$$

5- Read the current values shown by Ampermeters. Compare the current values in Ampermeters with the calculated current values.

6- Draw the phasor diagram and the impedance triangle of the circuit.



Figure 7.4

7- Find the circuit impedance using the values in measurement devices.

$$Z = \frac{E}{I} =$$

8- Find the power coefficient and phase angle of the circuit

$$\cos\varphi = \frac{IR}{E} =$$
$$\varphi =$$

9- Calculate the active power dissipated

$$P = E.I.\cos\varphi$$

$$P =$$