# **ELECTRONICS LABORATORY**

# PART 4

Assoc. Prof. Serhan Yarkan

**ISTANBUL COMMERCE UNIVERSITY** 

# Contents

TR	ANSISTORS	2
4	4.1 INTRODUCTION	2
4	4.2 OPERATION OF TRANSISTORS	2
	4.3 MEASUREMENT OF TRANSISTORS	6
	4.4 REGION I CHARACTERISTICS OF TRANSISTOR	9
	4.5 CALCULATIONS OF $\beta$ AND a CURRENT GAINS for TRANSISTORS	1 0
	4.6 LOAD LINE FOR A SPECIFIC RESISTANCE VALUE	11
	4.7 REGION II CHARACTERISTICS OF TRANSISTOR	.12
4	4.8 REGION III CHARACTERISTICS OF TRANSISTOR	.13
4	4.9 REGION IV CHARACTERISTICS OF TRANSISTOR	.14
4	4.9 REGION IV CHARACTERISTICS OF TRANSISTOR	14

# TRANSISTORS

#### **4.1 INTRODUCTION**

Transistor is the main circuit component in electronics. There are different transistors in terms of production type and working principle. Thus, they are defined with various names. Some of them are BJT, UJT, FET and MOSFET. We will examine BJT (**B**ipolar **J**unction **T**ransistor) in this chapter. In common usage, transistor means BJT.

BJT's are produced as NPN type by placing a thin P plate between two N plates or as PNP type by placing a thin N plate between two P plates. The material used in the middle has a thickness as much as 1/150 of total thickness. The symbols and structures of PNP and NPN type transistors are shown in Figure 4. 1



Figure 4.1

#### **4.2 OPERATION OF TRANSISTORS**



Figure 4. 2

The forward bias of PNP transistor's base-emitter terminals by supply  $E_{_{EB}}$  is shown in Figure 4. 2 PN combinations behaves like diode and current starts to pass. ( $E_{EB}$ , expresses the forward bias of PN combination. It is not valid to connect a direct supply to B-E terminals)



Figure 4. 3

The forward bias of PNP transistor's base-collector terminals by  $E_{BC}$  supply is shown in Figure 4. 3 P-N combination behaves like a diode.



Figure 4. 4

The inverse bias of PNP transistor's base-emitter terminals by supply  $E_{EB}$  is shown in Figure 4. 4 Compared to Figure 4. 2, it is observable that vacuumed region is widened and the passage of majority carriers is prevented. Minority flow occurs only at nA level of NP combination.



Figure 4. 5

The inverse bias of PNP transistor's base-collector terminals by supply  $E_{CB}$  is shown in Figure 4. 5 Compared to Figure 4. 3, it is observable that vacuumed region is widened and the passage of majority carriers is prevented. Minority flow occurs only at nA level of NP combination.

Now, let's apply the biases in Figure 4. 2 and Figure 4. 5 at the same time.



Figure 4. 6

It is observable from the width of the vacuumed region that which junction is forward biased and which junction is inverse biased. A small base current passes through the forward biased PN junction (**E-B**). Flow of a great magnitude of majority carrier starts between the collector-emitter terminals when the PN voltage set is broke. The initiator of the flow is the base current.

 $E_{BE}$  and  $E_{CB}$  supplies (connected to terminals E-C) are serial.  $E_{BE} + E_{CB}$  is applied to C-E terminals. Majority carrier flow starts between E-C as a result of base current passing. There is no current flow between B-C because B-C is inverse biased. If base current is cut during majority carrier flow it will stop forward bias of PN junction which forms E-B. So the vacuumed region of PN junction will be widened. Therefore, E-C current will also stop. Magnitude of  $I_C$  current depends on  $I_B$  current.  $I_E$  current is the sum of  $I_B$  and  $I_C$  currents. ( $I_E = I_B + I_C$ )

Let's see the operation of NPN transistor circuit:



Mid-terminal of potentiometer should be on chassis level.

So,  $E_{BE}=0$  and  $I_B=0$ .  $I_C$  depends on  $I_B$ , so  $I_C=0$ .

If the mid-terminal of potentiometer moved slowly to  $E_{CC}$  level than there will be an increasing  $I_B$ . Depending on  $I_B$ , there will be an  $I_C$  greater than  $I_B$ . Increase of  $I_C$  results in the increase of voltage on  $R_C$  resistor. Simultaneously,  $E_{CE}$  voltage decreases. If  $I_B$  is continued to increase  $I_C$  will also increase and  $E_{CE}$  will be approximately zero. At that value of  $E_{CE}$ ,  $I_C$  will be constant even if the  $I_B$  continued to increase. So the transistor will work at saturation (**that means the non-increase of I**<sub>C</sub>).

If the mid-terminal of potentiometer moved towards the chassis level,  $I_B$  will decrease and depending on it,  $I_C$  will also decrease and  $E_{CE}$  will increase. If  $I_B$  is zero (0) then  $I_C=0$  and  $E_{CE}=E_{CC}$  because there wont be voltage decrease on  $R_C$ 

Outside the cut-off and saturation situations of transistor, the ratio of  $I_C$  differences for different levels of  $I_B$  gives the current gain ratio of  $\beta$  (**beta**).  $I_B$ ,  $I_C$  and  $\beta$  values are as follows:

$$\beta = \frac{\Delta Ic}{\Delta Ib}$$
 Or  $\beta \cong \frac{Ic}{Ib}$ 

Outside the cut-off and saturation situations of transistor, the ratio of  $I_C$  differences for different levels of  $I_E$  gives the current gain ratio of  $\alpha$  (**alfa**).  $I_E$ ,  $I_C$  and  $\alpha$  values are as follows:

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$
 or  $\alpha \cong \frac{I_C}{I_E}$ 

 $\alpha$  (alfa) current gain is always lower than 1 (one).

Various types of transistor are shown in Figure 4.8.



Figure 4.8

### **4.3 MEASUREMENT OF TRANSISTORS**

Transistors, like diodes, can be measured by analog or digital avometers. Durability of transistor is measured by analog avometers through the resistance value between terminals; measured by digital avometers through the voltage value decrease by the current flowing between terminals. as we know, digital avometers are more reliable than analog. In avometer measurements, transistor is assumed to consist of two diodes. The equivalent circuits of PNP and NPN transistors are shown in Figure 4. 9. They are made of diodes.



Whatever the type of transistor, there are two diodes (opposite to each other) serially connected between the collector-emitter terminals. One of the resistances between the collector-emitter terminals is very big because one of two diodes is inverse biased. Because of that, there will not be any current flow. Whatever the bias of measurement there will be (**OL**) on display (just like there is no component between probes). Measurement in both ways between collector-emitter terminals are shown in Figure 4. 10



Figure 4. 10

The measurements to be made between base-collector and baseemitter are the same as diode measurement. Because of that, direction of bias is important. When "base=positive, collector=negative" and "base=positive, emitter=negative", diodes are forward biased. In forward bias, the resistance between base-collector terminals is low. When measuring with digital avometer, it is observed that a DC current flows from base to collector and from base to emitter. In silisium transistors "0,6Volt-0,7Volt" and in germanium transistors "0,1Volt-0,3Volt" is displayed on avometer. In Figure 4. 11, measurements of an NPN type silisium transistor at three forward biases are shown.



Figure 4. 11

Base-collector junction is larger than the base-emitter junction in the structure of transistor. As a result, the resistance between base-collector terminals is lower than resistance between base-emitter terminals. So, voltage between base collector terminals is lower than the voltage between the base-emitter terminals. It can be seen by the help of avometer.

When "base=negative, collector=positive" and "base=negative, emitter=positive", diodes are inverse biased. In inverse bias, the resistance between base-collector terminals and the resistance between base-emitter terminals are low. When making measurement with digital avometer, you will see the shape (OL) when there are no components between probes on display of avometer. Measurement at inverse bias is shown in Figure 4. 12



**Figure 4.12** 

If the measured transistor is an NPN type silisium transistor, the same results should be displayed when the direction of probes is opposite. If the results are not the same or very similar then the transistor is damaged.

#### **4.4 REGION I CHARACTERISTICS OF TRANSISTOR**

In a specific base current ( $\mathbf{I}_{B}$ =constant) of transistor, the curve ( $\mathbf{I}_{C}$ =f.( $\mathbf{V}_{CE}$ )) of change of collector current ( $\mathbf{I}_{C}$ ) depending on the collectoremitter voltage ( $\mathbf{V}_{CE}$ ) is called 1.region characteristics of transistor. This curve and the connection schema to derive that curve are shown in Figure 4. 13





Figure 4.13

Current gains of Beta ( $\pmb{\beta}$ ) and Alfa ( $\alpha$ ) can be calculated using the 1.region curve. Load line can be drawn according to a specific resistance value.

## 4.5 CALCULATIONS OF $\beta$ AND $\alpha$ CURRENT GAINS for TRANSISTORS

This method is used for calculating the current gains of small and potent transistors. Current gains in such transistors are same for a given  $V_{CE}$  voltage. As we know, beta ( $\beta$ ) current gain for a transistor with its emitter is chassis:

$$\beta = \frac{IC}{IB} = \frac{\Delta IC}{\Delta IB}$$

**Example:**  $\beta$  current gain of transistor is calculated as following. Assume that V<sub>CE</sub> voltage is constant at 5V; a perpendicular line is drawn from 5V upwards. In order to find I<sub>C</sub> currents, perpendicular lines are drawn from the points where that line intersects 10µA and 20µA base current curves. This is shown in Figure 4. 14



From characteristics curve:

$$I_{C2} = 1,5mA=1500\muA$$

$$I_{C1} = 0,7mA=700\muA$$

$$I_{B1} = 10\muA$$

$$I_{B2} = 20\muA$$

$$\Delta I_{C} = I_{C2}-I_{C1}=1500-700=800\muA$$

$$\Delta I_{B} = I_{B2}-I_{B1}=20-10=10\muA$$

$$\beta = \frac{\Delta I_c}{\Delta I_B} = \frac{800}{10} = 80$$

 $\alpha$  Current gain is calculated as following:  $\alpha = \frac{\Delta I_C}{\Delta I_C}$ 

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

The schema is used in calculating  $\beta$  current gain will also used here.

From characteristics curve:

 $\Delta I_{C}$ =  $I_{C2}$ - $I_{C1}$ =1500-700=800µA

 $\Delta I_{B}$ =  $I_{B2}$ -  $I_{B1}$ =20-10=10µA

 $\Delta I_{F} = \Delta I_{B} + \Delta I_{C} = 800 + 10 = 810 \mu A$ 

$$\alpha = \frac{\Delta I_c}{\Delta I_E} = \frac{800}{810} = 0,988$$

**NOT:**  $\alpha$  current gain in transistors is always smaller than 1.





In Figure 4. 15,  $V_{CC}$ =5V and  $R_L$ =1K $\Omega$ ; maximum current to pass through RL:

 $I_{C} max = V_{CC}/R_{L} = 5/1000 = 0,005A = 5mA.$ 

On characteristics, mark  $V_{CC}$ =5Volt on  $V_{CE}$  axis and  $I_{C}$  max=5mA on  $I_{C}$  axis. Link those two points with a line. This line is called load line and the mid-point of this line is work point.

### **4.7 REGION II CHARACTERISTICS OF TRANSISTOR**

In a specific collector-emitter voltage ( $V_{CE}$ =constant) of transistor, the curve ( $I_C$ =f.( $I_B$ )) of change of collector current ( $I_C$ ) depending on the base current ( $I_B$ ) is called 2.region characteristics of transistor. This curve and the connection schema to derive that curve are shown in Figure 4. 16.



Current gains of Beta  $(\boldsymbol{\beta})$  can be calculated benefiting from the 2.region curve.

### **4.8 REGION III CHARACTERISTICS OF TRANSISTOR**

In a specific collector-emitter voltage ( $V_{CE}$ =constant) of transistor, the curve ( $I_B$ =f.( $V_{BE}$ )) of change of base current ( $I_B$ ) depending on the base-emitter voltage ( $V_{BE}$ ) is called 3.region characteristics of transistor. This curve and the connection schema to derive that curve are shown in Figure 5. 17



Input impedance can be calculated using 3.region characteristics.

#### **4.9 REGION IV CHARACTERISTICS OF TRANSISTOR**

In a specific base current ( $I_B = constant$ ) of transistor, the curve ( $V_{BE} = f.(V_{CE})$ ) of change of base-emitter voltage ( $V_{BE}$ ) depending on the collector-emitter voltage ( $V_{CE}$ ) is called 4.region characteristics of transistor. This curve and the connection schema to derive that curve are shown in Figure 4. 18



Figure 4. 18

Voltage feedback ratio between collector-base can be calculated using the 4.region curve.