

# **ELECTRONICS LABORATORY**

## **PART 7 EXPERIMENTS**

**Assoc. Prof. Serhan Yarkan**

**ISTANBUL COMMERCE UNIVERSITY**

## Contents

<b>EXPERIMENT: 7.1</b> .....	2
EXAMINATION OF INTEGRATED SOUND AMPLIFIER.....	2
<b>EXPERIMENT 7.2</b> .....	4
EXAMINATION OF JFET'S INPUT CHARACTERISTICS.....	4
<b>EXPERIMENT 7.3</b> .....	7
EXAMINATION OF JFET.....	7
<b>EXPERIMENT 7.4</b> .....	8
EXAMINATION OF JFET.....	8

## EXPERIMENT 7.1

### EXAMINATION OF JFET'S INPUT CHARACTERISTICS

#### EXPERIMENTAL PROCEDURE:

Plug the Y-0016/012 module. Make the circuit connections as in Figure 7.1.

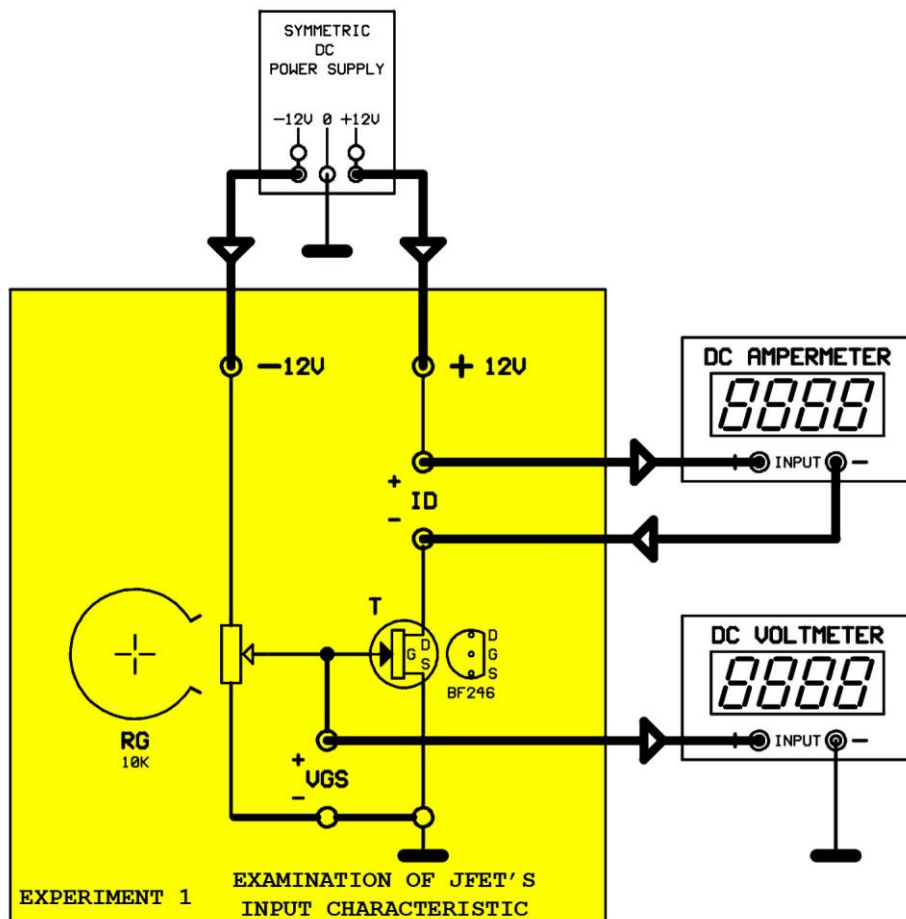


Figure 7.1

1- Type the VGS voltage to the table at Figure 7.2 with the help of RG potentiometer. Also type the ID values for each step.

$V_{DS}=12V$ CONSTANT	
$V_{GS}$ (VOLT)	$I_D$ (mA)
0.0	
-0.5	
-1.0	
-1.5	
-2.0	
-2.5	
-3.0	
-3.5	
-4.0	

Figure 7.2

2- Draw the VGS/ID curve using the values in Figure 7.2.

 


Figure 7.3

3- When the **VGS**=-3.5V or at a smaller value **ID**="0". What is the name for this value of VGS?

## EXPERIMENT: 7.2

### EXAMINATION OF JFET'S OUTPUT CHARACTERISTICS

#### EXPERIMENTAL PROCEDURE:

Plug the Y-0016/012 module. Before making the connections, adjust the output voltage of power supply to "0" by rotating voltage potentiometers to left. And adjust the gate voltage to "0" by rotating the "RG" potentiometer to left.

Make the circuit connections as in Figure 7.4 and apply energy to circuit.

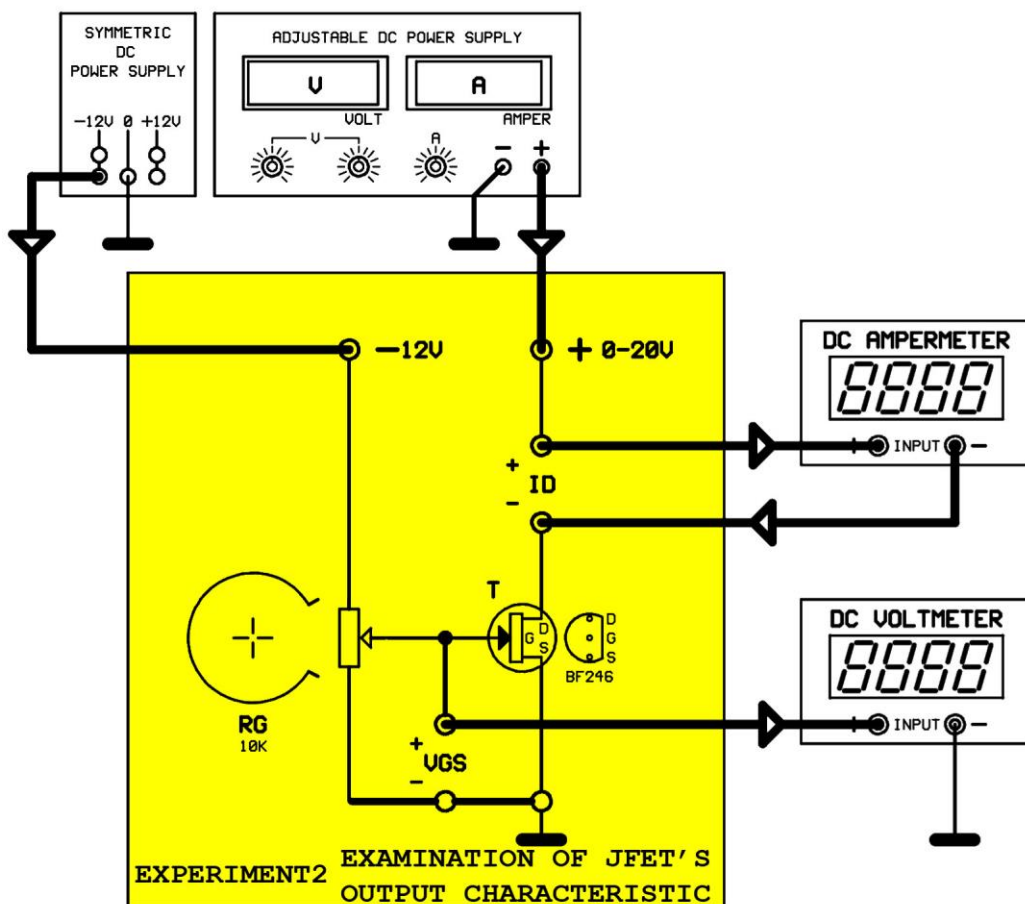


Figure 7.4


**1-** Set **VGS=0** using "**RG**" potentiometer. Adjust the power supply voltage to the VDS voltage values in Figure 7.5 and make sure that **VGS=0** at each step. Type the ID values at each step to section "**A**".

VGS=0 CONSTANT		VGS=-1 CONSTANT		VGS=-2 CONSTANT		VGS=-3 CONSTANT		VGS=-4 CONSTANT	
VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)
1		1		1		1		1	
2		2		2		2		2	
3		3		3		3		3	
4		4		4		4		4	
5		5		5		5		5	
10		10		10		10		10	
15		15		15		15		15	
20		20		20		20		20	

— A —
— B —
— C —
— D —
— E —

**Figure 7.5**

**2-** Draw change graphics between VDS/ID axes for each VGS voltage value.

 

**Figure 7.6**

**3-** ID is constant even if the VDS is increased. What is the name for this value of ID?


**4-** Adjust the VGS voltage to -1V, -2V, -3V, -4V, respectively. Adjust the VDS voltage to the values in Figure 7.11 and type each ID value next to each VDS value.

VGS=0 CONSTANT		VGS=-1 CONSTANT		VGS=-2 CONSTANT		VGS=-3 CONSTANT		VGS=-4 CONSTANT	
VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)	VDS (VOLT)	ID (mA)
1		1		1		1		1	
2		2		2		2		2	
3		3		3		3		3	
4		4		4		4		4	
5		5		5		5		5	
10		10		10		10		10	
15		15		15		15		15	
20		20		20		20		20	

—— A ——
—— B ——
—— C ——
—— D ——
—— E ——

**Figure 7.7**

**5-** Draw change graphics between VDS/ID axes for each VGS voltage value.

 

**Figure 7.8**

**6-** What is the name for these graphics?

**7-** Write the effect of gate bias to drain current.


**8-** Write the effect of VDS voltage to drain current.

## EXPERIMENT: 7.3

### EXAMINATION OF JFET
 
#### EXPERIMENTAL PROCEDURE:

Make the circuit connection and apply energy to circuit. You can use the same JFET that you used for previous experiment.



1 - Find the  $V_{GS1}$ ,  $I_{D1}$ ,  $V_{DS1}$ ,  $V_{GS2}$ ,  $I_{D2}$  and  $V_{DS2}$ .

2 - Plot the characteristics curve.




## EXPERIMENT: 7.4

### EXAMINATION OF JFET
 
#### EXPERIMENTAL PROCEDURE:

Make the circuit connection and apply energy to circuit. You can use the same JFET that you used for previous experiment.



1 - Find the  $V_{GS1}$ ,  $I_{D1}$ ,  $V_{DS1}$ ,  $V_{GS2}$ ,  $I_{D2}$  and  $V_{DS2}$ .

2 - Plot the characteristics curve.