

ELECTROTECHNICH LAB.

PART 4 EXPERIMENTS

Yrd. Doç. Dr. Taha İMECİ

Arş. Gör. Ezgi YAMAÇ

Arş. Gör. Ufuk ŞANVER

İSTANBUL COMMERCE UNIVERSITY

Contents

EXPERIMENT 17.1	2
EXAMINATION OF RL SERIES AC CIRCUIT	2
EXPERIMENT 17.2	5
EXAMINATION OF RC SERIES AC CIRCUIT	5
EXPERIMENT 17.3	8
EXAMINATION OF RLC SERIES AC CIRCUIT	8

EXPERIMENT 17.1

EXAMINATION OF RL SERIES AC CIRCUIT

REQUIRED MATERIAL:

- 1- Function Generator
- 2- Oscilloscope (**two channeled**)
- 3- AC voltmeter
- 4- AC ampermeter
- 5- Y-0016/01AC module
- 6- Enough connection cable

THE EXPERIMENT:

Adjust the terminal of the function generator to sine, peak to peak value to **E_{pp}**=10Volt and frequency to **F**=1KHz. Connect the Y-0016/01AC module to its place. Short-circuit the **J3**. Make the circuit connections as in the figure 16.5. Apply the power to the circuit.

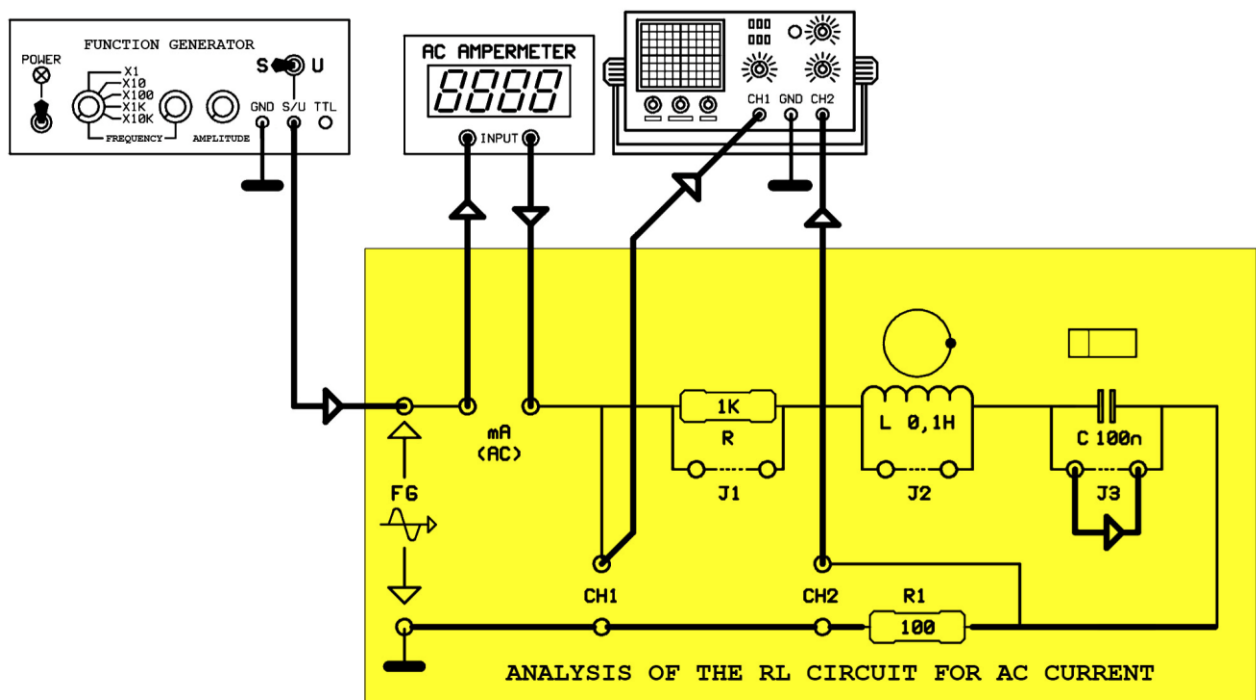


Figure 16.5

- 1- What is the effect of short-circuiting the **J3** points?

2- What can be said about the circuit looking at the vector diagram on the oscilloscope?

3- Calculate the inductive reactance of the inductor.

$$XL = 2\pi FL$$

4- Short circuit the CH2 points so that the "**R1**" resistor will not affect the circuit. Calculate the total resistance of the circuit.

5- Calculate the circuit impedance

$$Z^2 = RT^2 + XL^2$$

6- Calculate the circuit current.

7- Compare the current value in Ampermeter with the calculated current value.

8- Calculate the voltages on resistor and inductor using the current value (**2,6mA**).

$$ER = I.R =$$
$$EL = I.XL$$

9- Read the voltage values of resistor and inductor with the AC Voltmeter. Compare these values with the ones we calculated.

10- Calculate the circuit voltage using the calculated voltage values (ER and EL). Compare the result with the voltage (**E=3,5V**) that you applied to the circuit.

$$E^2 = ER^2 + EL^2$$

11- Draw the phasor diagram of the circuit and the impedance triangle.

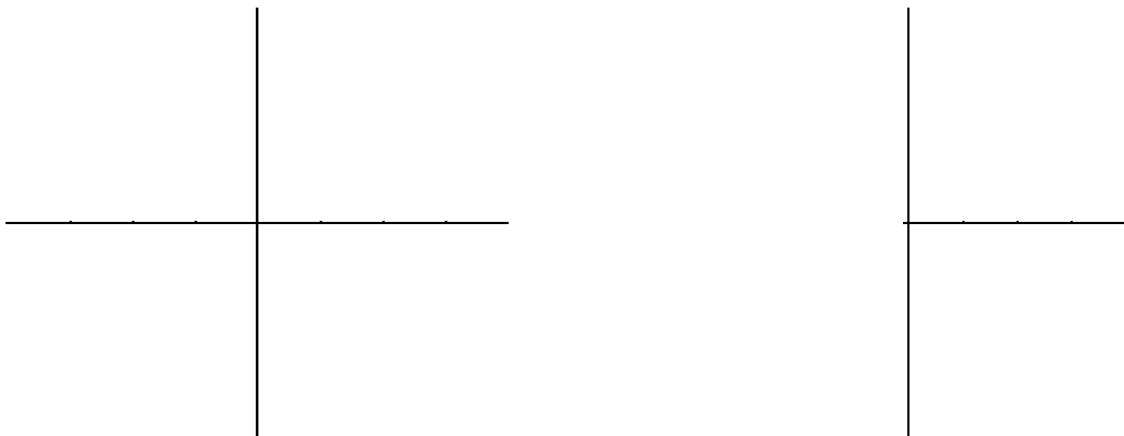


Figure 16.6

12- Calculate the power factor of the circuit, active power dissipated by the circuit and the phase angle.

$$\cos\phi = \frac{R}{Z} =$$

$$P = E.I.\cos\phi$$

EXPERIMENT 17.2

EXAMINATION OF RC SERIES AC CIRCUIT

REQUIRED MATERIAL:

- 1- Function Generator
- 2- Oscilloscope (**two channeled**)
- 3- AC voltmeter
- 4- AC ampermeter
- 5- Y-0016/01AC module
- 6- Enough connection cable

THE EXPERIMENT

Adjust the terminal of the function generator to sine, peak to peak value to **E_{pp}**=10Volt and frequency to **F**=1KHz. Connect the Y-0016/01AC module to its place. Short-circuit the **J2**. Make the circuit connections as in the figure 16.11. Apply the power to the circuit.

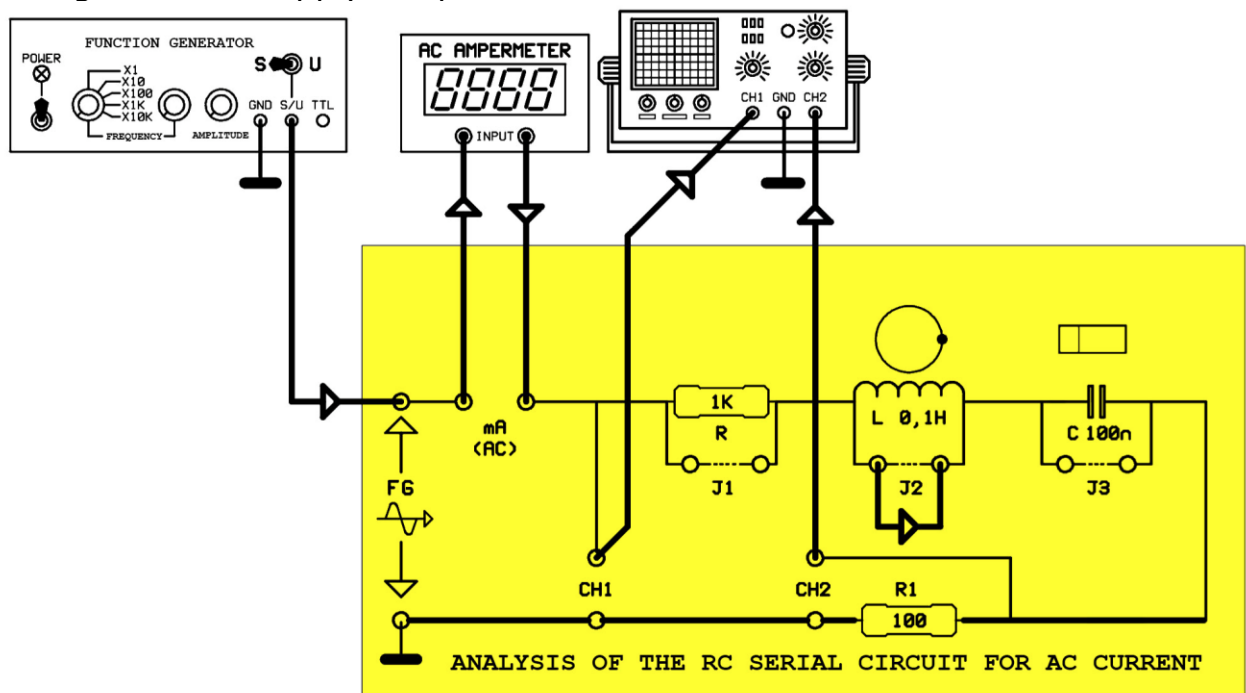


Figure 16.11

1- Why is the **J2** points short-circuited?

2- What can be said about the circuit looking at the vector diagram on the oscilloscope?

3- Short circuit the CH2 points so that the "**R1**" resistor will not affect the circuit. Calculate the total resistance of the circuit.

4- Calculate the capacitive reactance of the capacitor.

5- Calculate the circuit impedance.

$$Z^2 = RT^2 + XC^2$$

6- Calculate the circuit current.

7- Compare the current value in Ampermeter with the calculated current value.

8- Calculate the voltages on resistor and capacitor using the current value (**1,86mA**)

9- Read the voltage values of resistor and capacitor with the AC Voltmeter. Compare these values with the ones we calculated.

10- Calculate the circuit voltage using the calculated voltage values (ER and EL). Compare the result with the voltage (**E=3,5V**) that you applied to the circuit.

$$E^2 = ER^2 + EC^2$$

11- Draw the phasor diagram of the circuit and the impedance triangle.



Figure 16.12

12- Calculate the power factor of the circuit, active power dissipated by the circuit and the phase angle.

$$\cos\phi = \frac{R}{Z} =$$

$$P = E.I.\cos\phi$$

EXPERIMENT 17.3

EXAMINATION OF RLC SERIES AC CIRCUIT

REQUIRED MATERIALS:

- 1- Function Generator
- 2- AC voltmeter
- 3- AC ampermeter
- 4- Y-0016/01AC module
- 5- Enough connection cable

THE EXPERIMENT:

Adjust the terminal of the function generator to sine, peak to peak value to **E_{pp}**=10Volt and frequency to **F**=1KHz. Connect the Y-0016/01AC module to its place. Make the circuit connections as in the figure 16.17 Apply the power to the circuit.

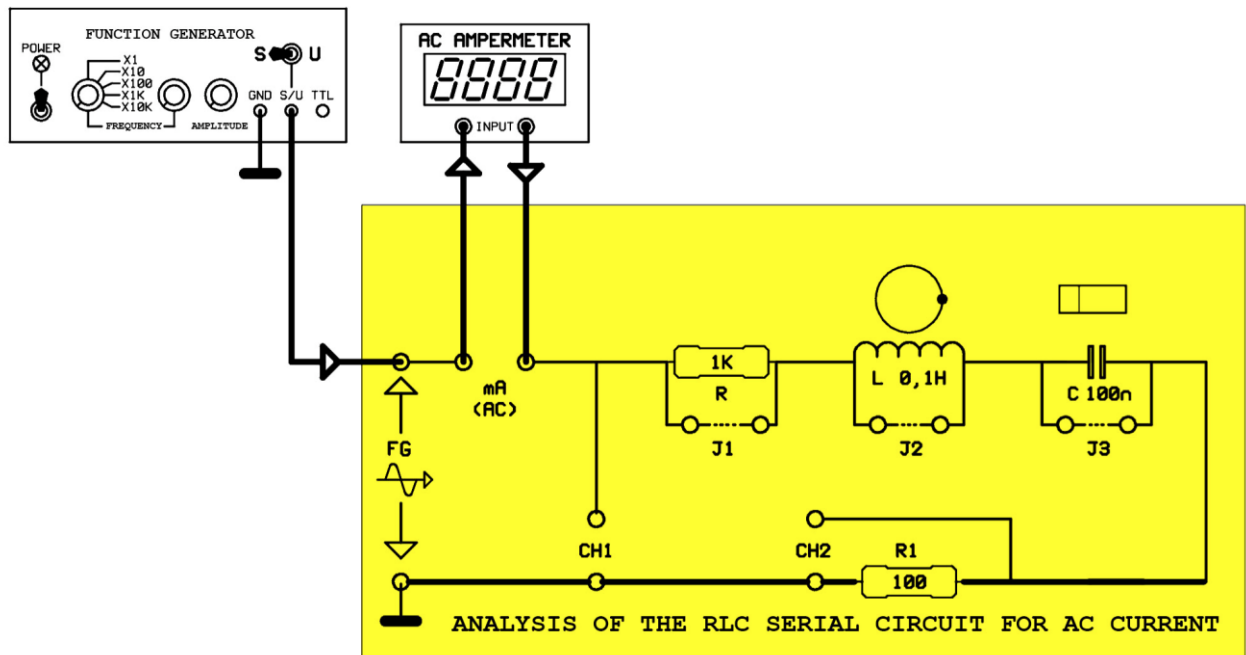


Figure 16.17

- 1- Short-circuit the CH2 points so that the "R1" resistor will not effect the circuit. Calculate the total resistance.

2- Calculate the inductive reactance of the inductor.

$$X_L = 2\pi FL$$

3- Calculate the capacitive reactance of the capacitor.

$$X_C = \frac{1}{2\pi FC}$$

4- Calculate the circuit impedance.

$$X_C > X_L$$

$$X_F = X_C - X_L =$$

$$Z^2 = R^2 + X_F^2$$

5- Calculate the circuit current.

6- Compare the current value in Ampermeter with the calculated current value.

7- Calculate the voltages on resistor, inductor and capacitor using the current value (**2,32mA**)

$$E_R = I.R =$$

$$E_L = I.X_L =$$

$$E_C = I.X_C$$

8- Read the voltage values of resistor, inductor and capacitor with the AC Voltmeter. Compare these values with the ones we calculated.

9- Calculate the circuit voltage using the calculated voltage values (E_R , E_C and E_L). Compare the result with the voltage (**$E=3,5V$**) that you applied to the circuit

$$E_C > E_L$$

$$E_F = E_C - E_L$$

$$E^2 = E_R^2 + E_F^2$$

10- Draw the phasor diagram of the circuit and the impedance triangle.



Figure 16.18

11- Calculate the power factor of the circuit, active power dissipated by the circuit and the phase angle.

$$\cos\phi = \frac{R}{Z} =$$

$$P = E.I.\cos\phi$$