

**ISTANBUL COMMERCE UNIVERSITY**  
**SPRING 2013-2014 / EEE / ELECTROTECHNIC LAB. / FINAL**  
**OPEN-ACCESS COPY (29.04.2015)**  
**(SOME QUESTIONS WERE CUTTED)**

**NAME** : .....

**ID** : .....

**SIGNATURE:** .....

Total	
Q1	
Q2	
Q3	
Q4	
Q5	
Q6	
Q7	

- Put your full name and student ID on every page.
- Read all questions carefully. There should be 4 separate pages with questions written on them.
- You can start from any question. You can use both sides of the paper to compile your answer.
- You may NOT ask help from proctors.
- Laboratory notes or experiment pages are NOT allowed.
- Talking, or using any device (calculator, mobile phone etc.) are prohibited.
- If you get caught cheating, you will forfeit the entire exam.
- Exam Duration: ... **min.**

Res. Asst. Ezgi Yamaç

Good luck!

Res. Asst. Ufuk Şanver

Assoc. Prof. Taha İmeci

**Q1(10p).** Write value of resistances.

**R1** : Red + Red + Red + Gold = .....**Ω** ±.....%

....

**R10** : Red+ Red+ Black+ Orange+ Silver = .....**K** ±.....%

COLOUR	VALUE
BLACK	0
BROWN	1
RED	2
ORANGE	3
YELLOW	4
GREEN	5
BLUE	6
VIOLET	7
GREY	8
WHITE	9

COLOUR	TOLERANCE
BROWN	±1.00%
RED	±2.00%
GREEN	±0.50%
BLUE	±0.25%
VIOLET	±0.10%
GREY	±0.05%
GOLD	±5.00%
SILVER	±10.00%


NAME : .....

ID : .....

**Q2(20p).** Mark the statements below true (T) or False (F).

- \_\_\_\_\_ a) Current.: Denoted by I, measured in Amperes (A).
- \_\_\_\_\_ b) Resistance.: Denoted by R, measured in volts (V) .
- ....
- \_\_\_\_\_ s) Internal resistance of a voltmeter is very high.
- \_\_\_\_\_ t) An oscilloscope is connected serially to the circuit.

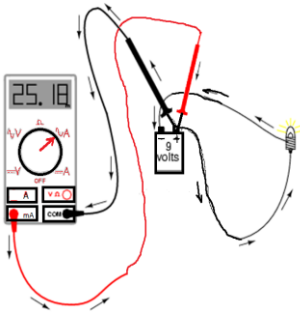**Q3(4p).** Re-draw the correct shape (for ampermeter).




NAME : .....


ID : .....

**Q4(10p).**

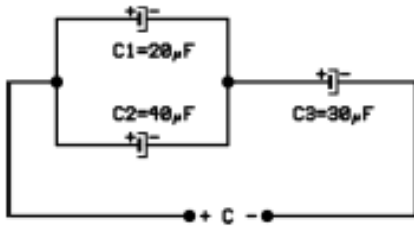
a) Calculate the total capacitance of the circuit shown below.



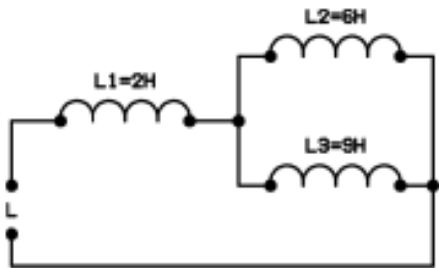b) Calculate the total inductance of the circuit shown below.



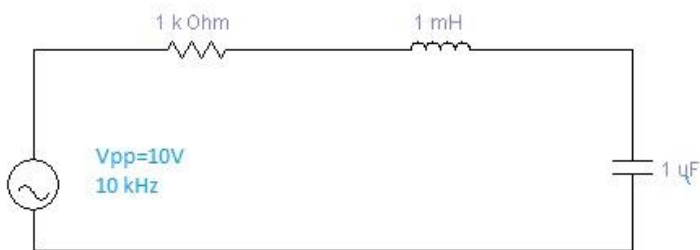**Q5(11p).** Use the circuit shown to fill in the table below and connect an ammeter and a voltmeter into the right position on the circuit to measure voltage and the current of the resistor. (internal resistor of the coil is zero.)




For each circuit element find	R (1K)	L (1mH)	C (1µF)
Effective Current (A)			
Effective Voltage (V)			
Power (W)			

**NAME** : .....

**ID** : .....

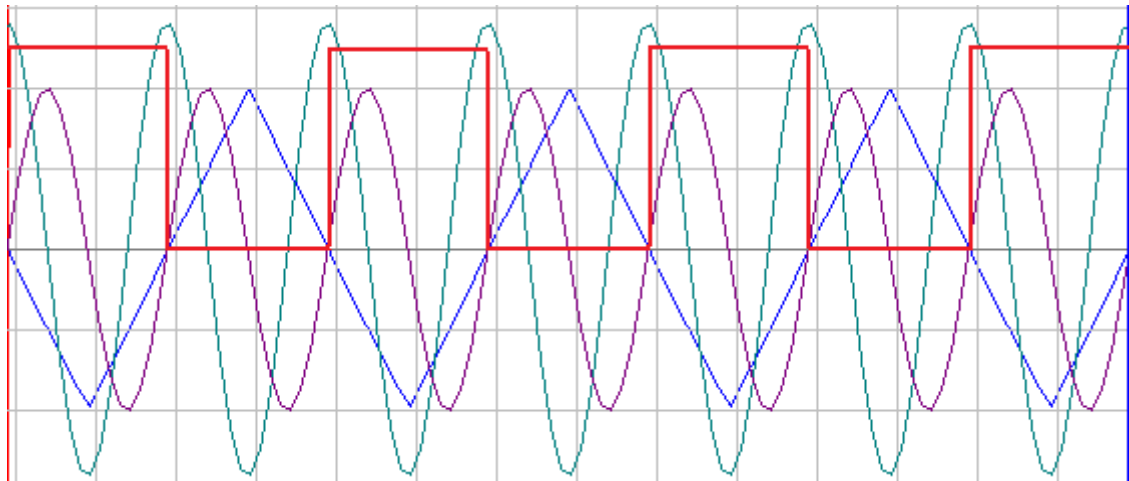**Q6(40p).** Use the oscilloscope screen shown to fill in the table below.



	<b>CHA</b>	<b>CHB</b>	<b>CHC</b>	<b>CHD</b>
<b>Time/Div:</b>	10ms	5us	5ms	5ms
<b>Volts/Div:</b>	5V	10V	5V	5V
<b>Signal</b>	Square Wave	Triangle Wave	Sinusoidal Wave	Sinusoidal Wave
f (Hz)				
V <sub>max</sub> (V )				
V <sub>min</sub> (V )				
V <sub>p-p</sub> (V )				
V <sub>average</sub> (V )				

**Q7(5p).** Calculate the phase difference between CHC and CHD.