

ELECTRONICS LAB.

PART 6 EXPERIMENTS

Yrd. Doç. Dr. Taha İMECİ

Arş. Gör. Ezgi YAMAÇ

Arş. Gör. Ufuk ŞANVER

İSTANBUL COMMERCE UNIVERSITY

Contents

| | |
|--|----------|
| EXPERIMENT: 6.1 | 2 |
| EXAMINATION OF CLASS A AMPLIFIER | 2 |
| EXPERIMENT: 6.2 | 4 |
| EXAMINATION OF CLASS B AMPLIFIER | 4 |
| EXPERIMENT: 6.3 | 6 |
| EXAMINATION OF CLASS C AMPLIFIER | 6 |

EXPERIMENT: 6.1

EXAMINATION OF CLASS A AMPLIFIER

EXPERIMENTAL PROCEDURE:

Plug the Y-0016-010 module. Make the circuit connection as in figure 15.4

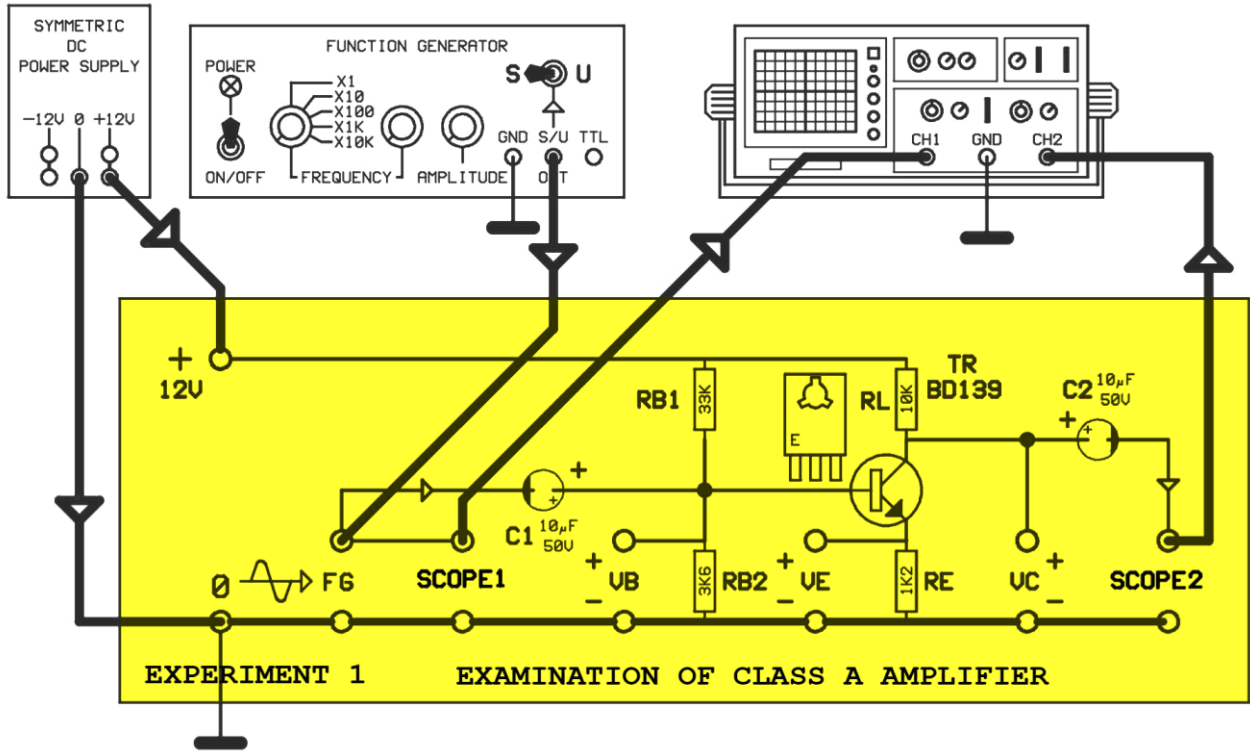


Figure 15.4

Note: Voltmeters are not shown in circuit connection schema. Make the voltage measurements for the related part by using a digital voltmeter.

1- Turn of the function generator. Apply energy to the circuit. Measure the voltages on transistor terminals (**VE-VB-VC**) and type them. How is the transistor according to these values?

| | | |
|--------------------------|------------|---|
| Emitter voltage | VE= | V |
| Base voltage | VB= | V |
| Collector voltage | VC= | V |

2- Adjust the amplitude potentiometer of function generator to zero (**mid-terminal will be at left**). Apply energy to function generator. Adjust the function generator's output signal to sine wave, frequency to 1KHz and amplitude to peak to peak **V_{ipp}=1Volt**. See the input and output signals at oscilloscope.

3- How is the phase relation between input and output signals? Why?

4- Is the form of output signal the same as input signal? Compare two signals.

5- What can be said about the productivity of class A amplifiers?

EXPERIMENT: 6.2

EXAMINATION OF CLASS B AMPLIFIER

EXPERIMENTAL PROCEDURE:

Plug the Y-0016-010 module. Make the circuit connections as in figure 15.7

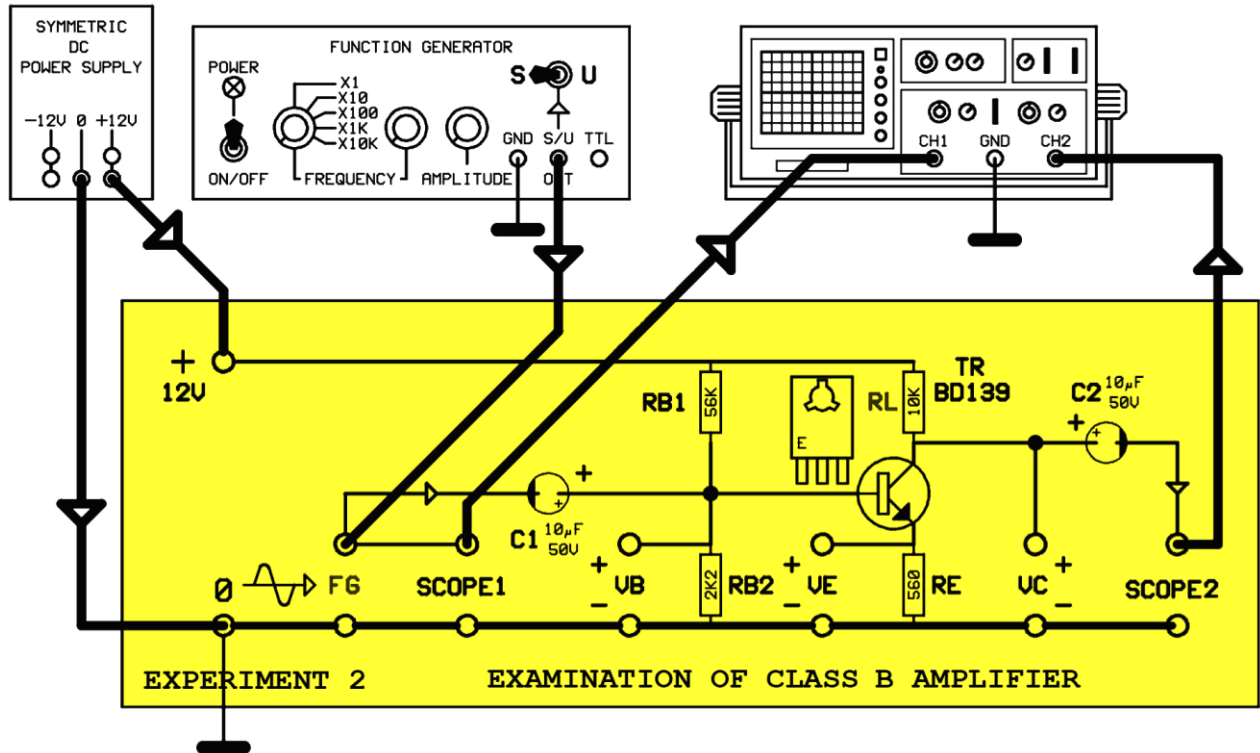


Figure 15.7

Note: Voltmeters are not shown in circuit connection schema. Make the voltage measurements for the related part by using a digital voltmeter.

1- Turn of the function generator. Apply energy to the circuit. Measure the voltages on transistor terminals (**VE-VB-VC**) and type them. How is the transistor according to these values.

| | | |
|--------------------------|------------|----|
| Emitter voltage | VE= | mV |
| Base voltage | VB= | V |
| Collector voltage | VC= | V |

VF=VB-VE=

2- Adjust the amplitude potentiometer of function generator to zero (**mid-terminal will be at left**). Apply energy to function generator. Adjust the function generator's output signal to sine wave, frequency to 1KHz and amplitude to peak to peak **V_{ipp}=1Volt**. See the input and output signals at oscilloscope.

3- Is the form of output signal the same as input signal? Compare two signals.

4- What can be said about the productivity of class B amplifiers?

EXPERIMENT: 6.3

EXAMINATION OF CLASS C AMPLIFIER

DENEYİN YAPILIŞI:

Plug the Y-0016-010 module. Make the circuit connections as in figure 15.10

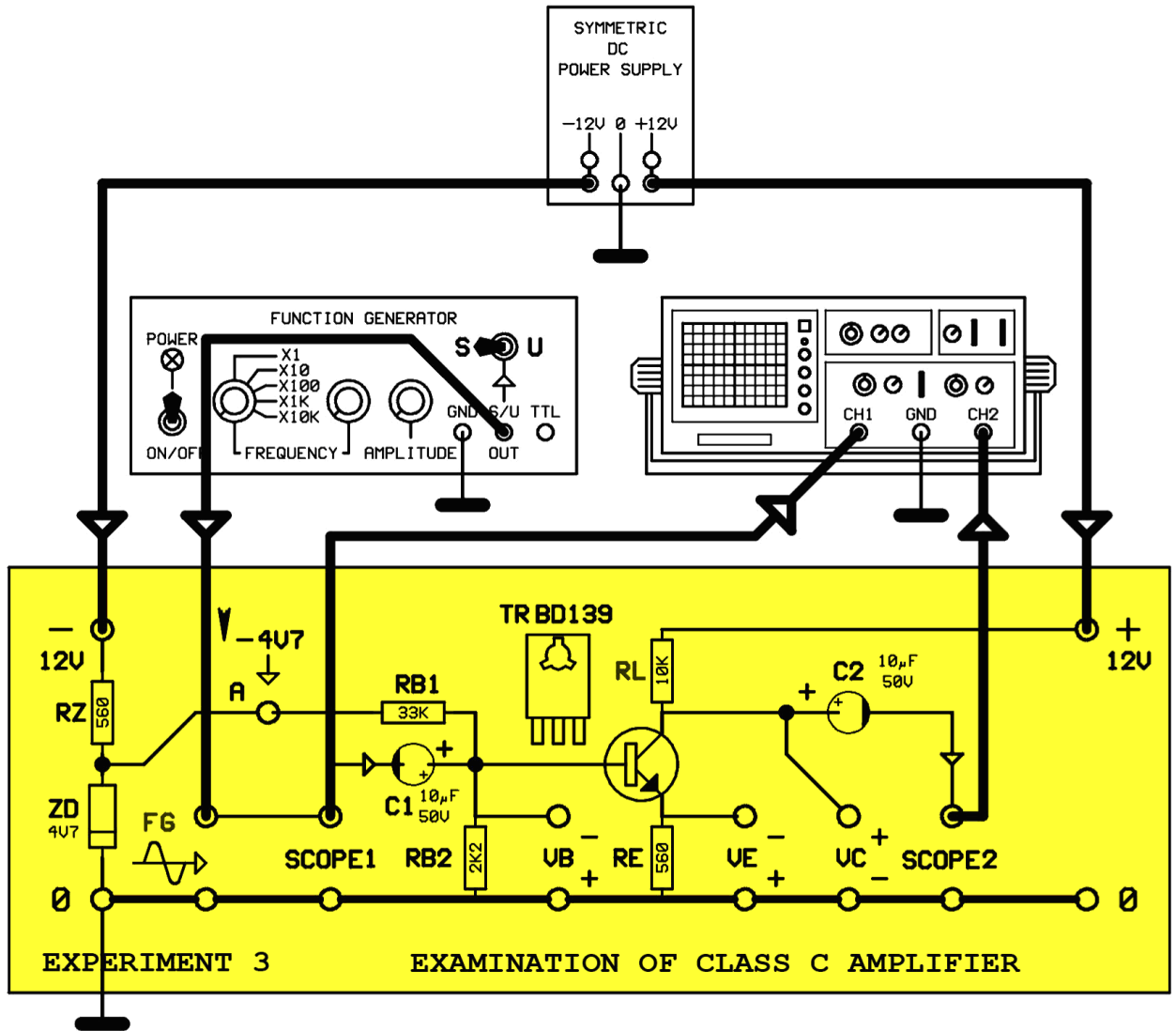


Figure 15.10

Note: Voltmeters are not shown in circuit connection schema. Make the voltage measurements for the related part by using a digital voltmeter

1- Turn of the function generator. Apply energy to the circuit. Measure the voltages on transistor terminals (**VE-VB-VC**) and type them. How is the transistor according to these values?

| | | |
|--------------------------|------------|-----------|
| Emitter voltage | VE= | <i>mV</i> |
| Base voltage | VB= | V |
| Collector voltage | VC= | V |

2- Adjust the amplitude potentiometer of function generator to zero (**mid-terminal will be at left**). Apply energy to function generator. Adjust the function generator's output signal to sine wave, frequency to 1KHz and amplitude to peak to peak **Vipp=3Volt**. See the input and output signals at oscilloscope.

3- Is the form of output signal the same as input signal? Compare two signals.

4-What can be said about the productivity of class C amplifiers