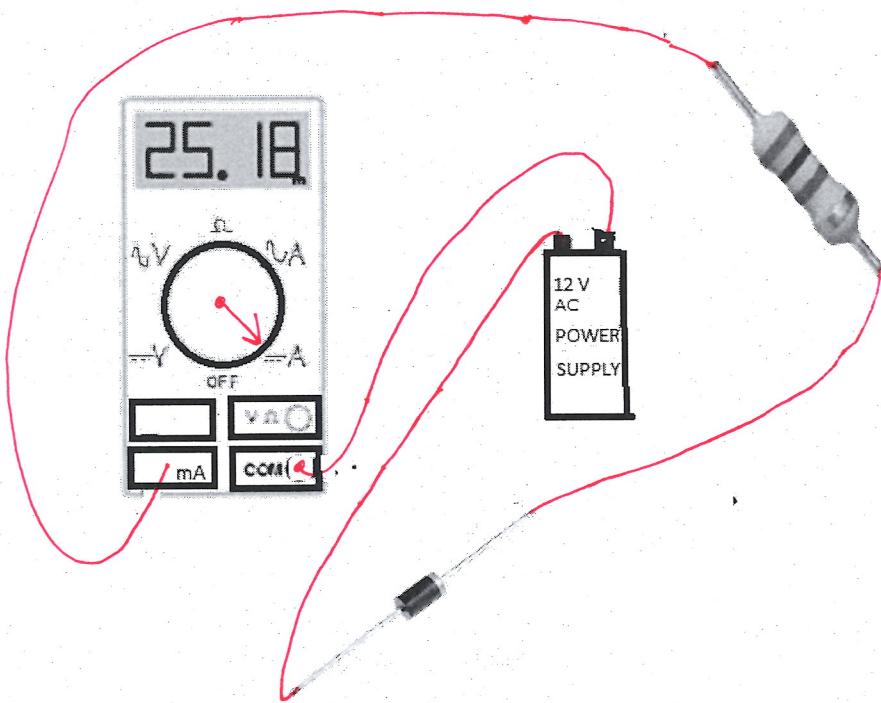


## Electronics Lab

Q1

- a) Connect the resistor, diode, power supply to built a half wave rectifier circuit and measure the DC output current with using the multimeter. (AC Power Supply 12V RMS, 1Hz, RL=1K)



- b) What is the approximately maximum and minimum voltage values (Vmax) of input (AC Power Supply) and output (RL) signals ?


$$V_{max} = V_{in} \sqrt{2}$$

$$V_{max} \text{ for input} = 12 \cdot \sqrt{2} = 12.14 = 16.8V \quad V_{max} \text{ for output} = 16.8V$$


$$V_{min} \text{ for input} = -16.8V$$

$$V_{min} \text{ for output} = 0V$$

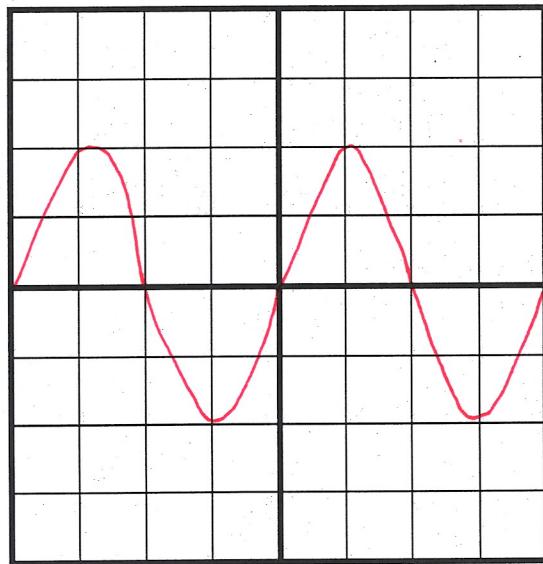- c) We connect CH1 of oscilloscope to AC Power Supply and CH2 of oscilloscope to RL.  
 Draw the signals, which we can see in osilosope.  
 You should write the oscilloscope volts/div and times/div values and draw the signals scaled.



Volts /div 8,4V CH1 Times /div 250ms

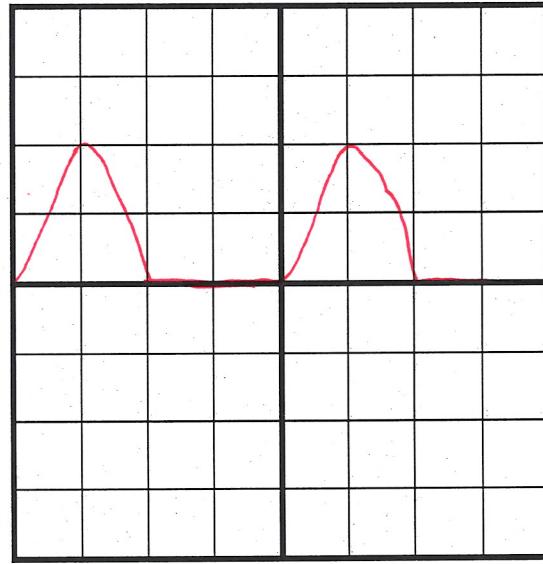


Volts /div 8,4V CH2 Times /div 250ms


- d) Calculate the mean DC output voltage and mean DC output current of the circuit.

$$V_{DC \text{ mean}} = \frac{V_{max}}{\pi} \rightarrow \frac{16,8V}{3} = 5,6V \quad I_{DC \text{ output}} = \frac{5,6V}{1k} = 5,6mA$$

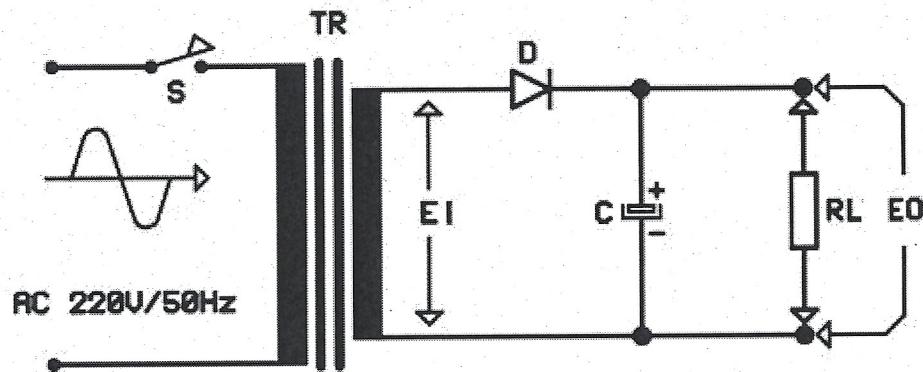**Q2** RL resistance is connected to an oscilloscope.



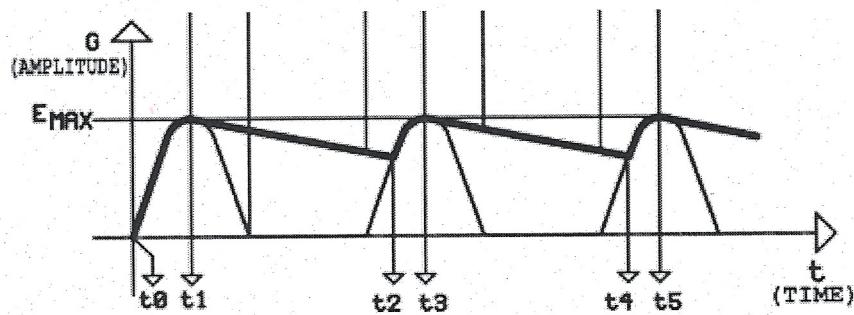- a) (5p) Draw the output voltage roughly (E0)




(5p) If the value of C increases, how does the peak to peak value of ripple voltage of E0 change? Why?


The peak to peak voltage decreases. Because time constant changes. (Time constant increases)

Q3 Draw the  $I_C$  vs  $V_{CE}$  characteristics (do not forget to entitle axis) using the values given in table and calculate the beta current gain using table. (Note: Units of IC is mA)

IB=20mA CONSTANT		
ORDER	UCE(V)	IC
1	0,02	0,06
2	0,04	0,19
3	0,06	0,35
4	0,08	0,54
5	0,10	0,70
6	0,50	1,37
7	1,00	1,95
8	2,00	2,30
9	4,00	2,32
10	6,00	2,32
11	8,00	2,32
12	10,00	2,32

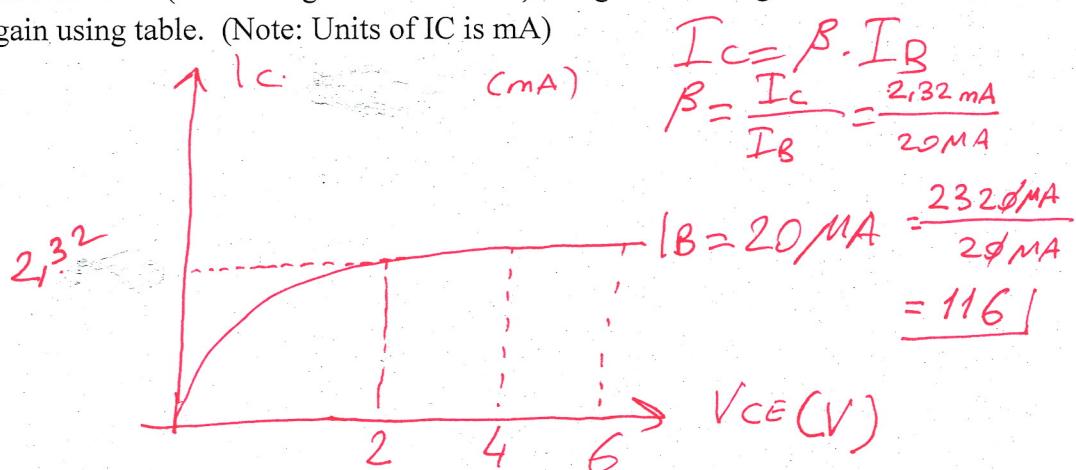

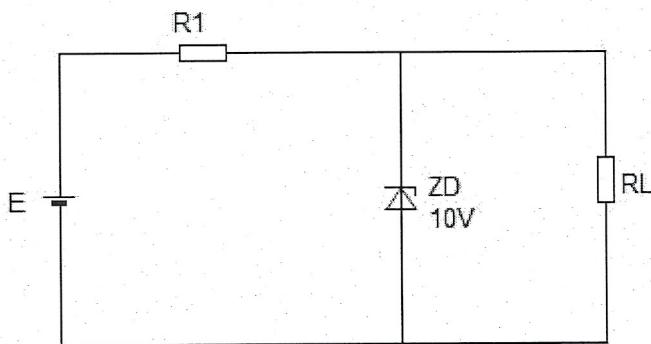Q4 Answer the questions with using Figure.  $R_1=100 \text{ Ohm}$ ,  $R_L=400 \text{ Ohm}$ .



a) Calculate and fill the table.

	IR1 (mA)	IRL (mA)	VR1 (V)	VRL (V)
For $E=5V$	10	10	1V	4V
For $E=14V$	40	25	4	10

For  $E=5V$

$$IR_1 = I_{RL} = \frac{5V}{100 + 400} = \frac{5V}{500 \text{ ohm}} = 10 \text{ mA}$$

$$V_{RL} = 100 \cdot 10 \text{ mA} = 1V$$

$$V_{RL} = 5V - 1V = 4V$$

For  $E=14V$


$$IR_1 = \frac{14V - 10V}{R_1} = \frac{4V}{100 \text{ ohm}} = 40 \text{ mA}$$

$$V_{RL} = 10V$$


$$I_{RL} = \frac{10V}{400 \text{ ohm}} = \frac{10 \cdot 0.001 \text{ A}}{400 \text{ ohm}} = 25 \text{ mA}$$

$$V_{RL} = 14V - 10V = 4V$$

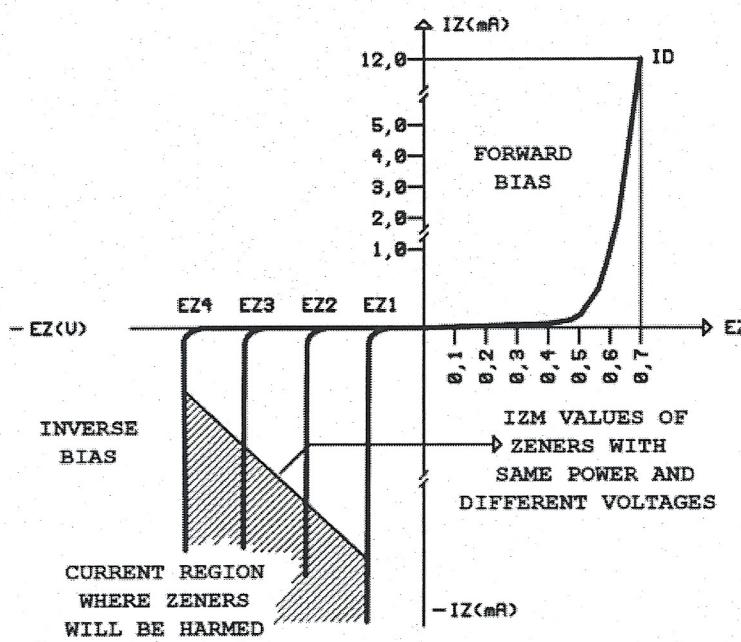b) Draw the full characteristics of zener diode ( $V_z$ - $I_z$  graphics)



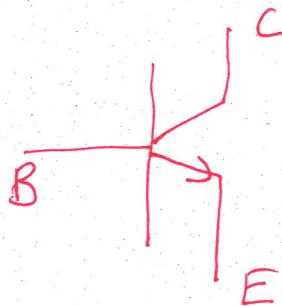Q5 Draw a symbol of NPN BJT Transistor and sign the emitter, collector and base pins on it.



Q6 Draw a voltage tripler.

